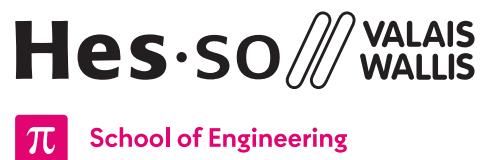




RC-Car (KART)

Lecture Summerschool 1 (SS1)



Orientation: Systems Engineering (Synd)

Specialisation: Infotronics (IT)

Course: Summerschool 1 (SS1)

Authors: Silvan Zahno, Axel Amand, François Corthay, Charles Praplan

Date: 25.06.2024

Version: v1.0



Contents

1 Security Guide	5
1.1 Consequences	6
2 Introduction	7
2.1 Objective	7
2.2 Evaluation	7
2.3 Files	7
2.4 Tools	8
2.5 Cabling	9
3 System Architecture	10
3.1 Block diagram	11
3.2 Functions	12
4 Hardware Components	13
4.1 Good Practices	14
4.2 Motherboard (MB)	14
4.2.1 Power	14
4.2.1.1 Charging	14
4.2.1.2 Power-on	14
4.2.1.3 Power State	15
4.2.2 SODIMM Daughterboard Connector	15
4.2.3 I/Os	15
4.2.4 FPGA Reset	16
4.2.5 UART Sniffer	16
4.2.6 BLE Socket	16
4.3 Dautherboard (DB)	17
4.3.1 Power	17
4.3.2 Programming	17
4.3.3 Connection with Motherboard	17
4.3.4 I/O	18
4.4 Motors	19
4.4.1 DC-Motor	19
4.4.2 Stepper-Motor	19
4.4.3 PMOD DC-Stepper Control board	20
4.5 End of turn switch	21
4.6 Hall Sensor	21
4.7 Bluetooth Dongle NRF52840	22
4.8 Sensor & I/O	22
4.8.1 Servo Motor	22
5 FPGA Design	23
5.1 DC Motor Controller	24
5.1.1 Functionality	24
5.1.1.1 PWM Generation	25
5.1.1.2 Hardware orientation	25
5.1.2 Bluetooth connection	25



5.1.3 Tests	25
5.2 Stepper Motor Controller	26
5.2.1 Functionality	26
5.2.2 Driving coils	26
5.2.3 Zero position	27
5.2.4 Hardware orientation	27
5.2.5 Initial position	28
5.2.6 Tests	28
5.3 Sensors Controller	29
5.3.1 Functionality	29
5.3.2 Hall counter	30
5.3.2.1 Tests	30
5.3.3 Ultrasound Ranger (<i>Optional</i>)	31
5.3.3.1 Tests	31
6 Testing	32
6.1 Per module	33
6.1.1 DC Motor testing	33
6.1.1.1 Testing	33
6.1.2 Stepper Motor testing	35
6.1.2.1 Testing	35
6.1.3 Sensors Controller testing	37
6.1.3.1 Testing	37
6.2 Whole circuit	38
6.2.1 Modules Simulation	38
6.2.1.1 Tests	40
6.2.2 Full-board	40
6.3 Programming the board	40
6.4 USB commands emulation	41
6.4.1 Quick Test	41
6.4.2 Registers R/W	42
7 Communication	43
7.1 General Principle	44
7.1.1 Serial Port Configuration	44
7.1.2 Message format	44
7.1.2.1 Frame example	44
7.2 Registers	45
7.3 Initialisation Sequence	47
A Tools	48
A.1 HDL Designer	48
A.2 Modelsim	49
A.3 Microchip Libero	50
A.3.1 Overview	50
A.3.1.1 Synthesis	50
A.3.1.2 Flash	50
A.3.2 Synthesis	51
A.3.2.1 Prepare project	51
A.3.2.2 Synthesize	52



A.3.2.3 Bitfile	53
A.3.2.4 Tips	53
A.3.3 Flashing	54
A.3.3.1 FlashPro	54
A.3.3.2 OpenOCD	55
B PMod boards	56
B.1 Inputs	56
B.1.1 Ultrasound Ranger	56
B.1.2 Buttons / Digital Inputs	57
B.2 Outputs	57
B.2.1 PMOD-OD2 board	58
B.2.2 Simple 4 Leds or Digital Outputs	59
B.3 Breadboard	60
C Inspiration	61
Bibliography	66



1 | Security Guide

In the pursuit of creating a small remote-controlled car, it is imperative to consider the security-aspect of the project. Ensuring the integrity of the hardware, preventing damage to components and personal safety are vital. This chapter outlines the security measures and protocols that must be adhered to throughout the course of the project. These measures have been put in place to protect both the project's hardware and the participants involved.

Some security rules are also mentioned again in the following chapters, where they are relevant.



Think before doing

Certainly, thinking before taking action is a fundamental principle of effective project management and security.



No Hardware to Leave the Premises

To safeguard the project's hardware components, it is strictly forbidden for any team member to take project-related hardware home.

All hardware must be properly stored in the designated laboratory cabinets.



Behaviour in the Labors

To safeguard the project's hardware components, it is strictly forbidden to have any food and drinks close to the project-related hardware.

In addition protection for other equipments such as tables, instruments must be used.

The Labors needs to be kept clean and tidy.



Mechanical Precautions

The motors used in the remote-controlled car can pose a physical risk, and special attention should be given to prevent accidents and injuries. Team members must exercise caution when handling the motors, ensuring that they are properly secured, and that all moving parts are well-guarded to prevent accidental contact.



Personal Protective Equipment (PPE)

When working with mechanical tools and machines, it's imperative to prioritize the safety of all team members. PPE, such as safety goggles, gloves, ear protection, and dust masks, should be worn as appropriate when operating machinery. Always remember, safety first.



Power Disconnection Protocol

Completely disconnect any power source before making changes or modifications on the hardware.



Battery Precautions

Before connecting batteries to the remote-controlled car, comprehensive functional testing is mandatory. The following precautions must be taken:

- Prior to connecting the batteries, all functionalities of the car must be tested using a laboratory power supply limited to $0.05A$, excluding the motors. When attaching the motors and other custom equipment, the power supply limit must be increased to $1.2A$. This precaution prevents sudden surges of current from damaging the circuitry during the initial testing phase.
- Make sure to shut the circuit off before charging to avoid higher voltages on the $12V$ rail. The charge rate should be around $0.4C \Rightarrow 1500mA$ here. Use only dedicated Ni-Mh chargers.



Secure SODIMM Connector

The FPGA board is a critical component of the remote-controlled car project. To ensure its proper functioning, the SODIMM connector must be inspected at each test to verify that the FPGA board is securely connected. Loose connections can result in system malfunctions, data corruption, and potential damage to the FPGA.



Help is available

In case of any questions or concerns regarding the security of the project, the team members are encouraged to contact assistants and professors.

1.1 Consequences

It is crucial to emphasize that any deviation from the security measures outlined in this chapter will result in consequences. It will involve the **deduction of points from the final project grade**. This penalty serves as a reminder of the importance of adhering to the security protocols and maintaining the integrity of the project.

In conclusion, security is a paramount consideration in the development of the remote-controlled car project. The security measures presented in this chapter are designed to protect the hardware and people, prevent damage, and ensure the project's success. By following these protocols and cooperating with professors, the team can create a safe and secure environment for project development while minimizing the risk of damage.



2 | Introduction

The Kart module (SS1) is a Summer School module for students between the 2nd and the 3rd semester. It is a home-made model car remotely controlled by a smartphone. The Appendix C - [Inspiration](#) gives an overview of previous year's karts.

The work of the students can be summarized in four main tasks:

- design and assembly of the chassis and the body
- analysis of the Direct Current (DC) motor [1]
- configuration of the controlling Field Programmable Gate Array (FPGA) [2]
- completion and extension of the control Graphical User Interface (GUI) on the smartphone

This document only covers the configuration and programming of the control electronics.

2.1 Objective

For the control electronics part there are three mandatory objectives:

- Control block for the DC Motor, see Section 5.1 - PWM Modulator
- Control block for the stepper motor, see Section 5.2 - 4 coils sequence generator
- Hall-Sensor counter, see Section 5.3

2.2 Evaluation

Fullfilling all mandatory objectives mentioned in Section 2.1 will result in a grade of 4.0. The students are free to implement additional features. For every added feature, the grade will be increased. Depending on the complexity of the feature between 0.5 and 1.0. until the maximum grade of 6.0 is reached.

Optional features can be:

- Emergency Stop using an ultrasonic distance sensor
- Animate Kart parts with servomotors and others I/Os
- Other improvements outside the scope of the predefined objectives

2.3 Files

All necessary files can be collected via two methods:

1. Either downloaded via a zip file at the following link <https://github.com/hei-synd-ss1/ss1-vhdl/archive/refs/heads/main.zip> [3] directly from github and extract it into your preferred location.
2. Alternatively a group specific repository can be created via github classroom by using the following invitation link: <https://classroom.github.com/a/pgjx0vpr>. Your repository can then be cloned with **git**.

```
git clone https://github.com/hei-synd-ss1-stud/2024-ss1-vhdl-<groupname>.git
```



Make sure there is no space characters in the full projects path. HDL may hang while booting or files may not be loaded/saved correctly.



2.4 Tools

The design environment for the control electronic consists of several tools.

- Mentor HDL designer for graphical design entry [4]

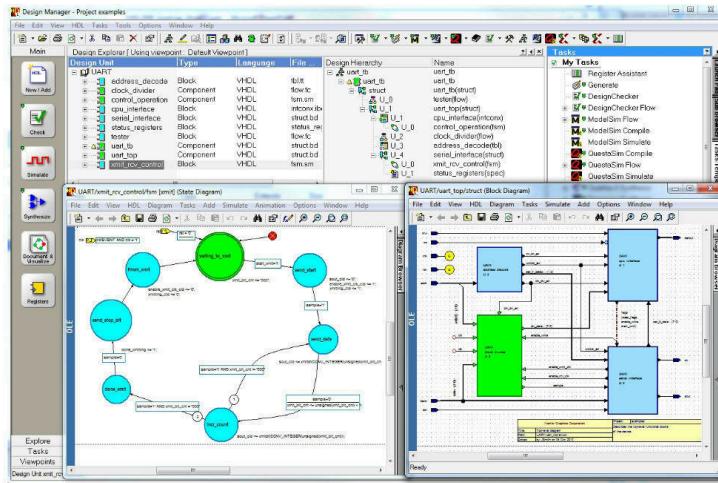


Figure 1: Mentor HDL Designer

- Mentor ModelSim for simulation [5]

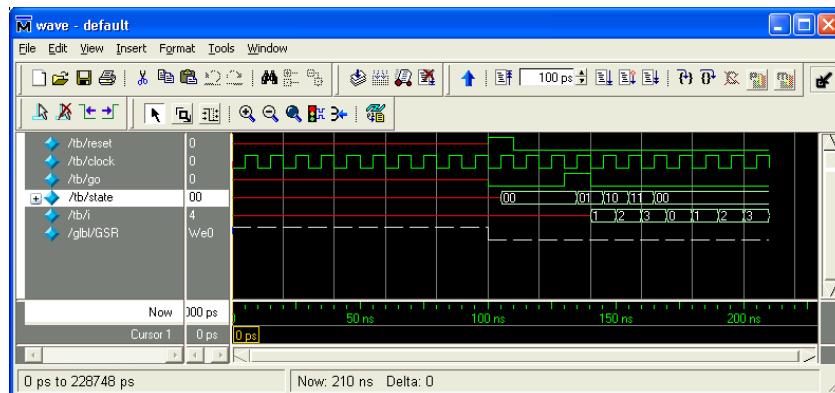


Figure 2: Mentor Modelsim

- Microchip Libero IDE for synthesis and programming[6]

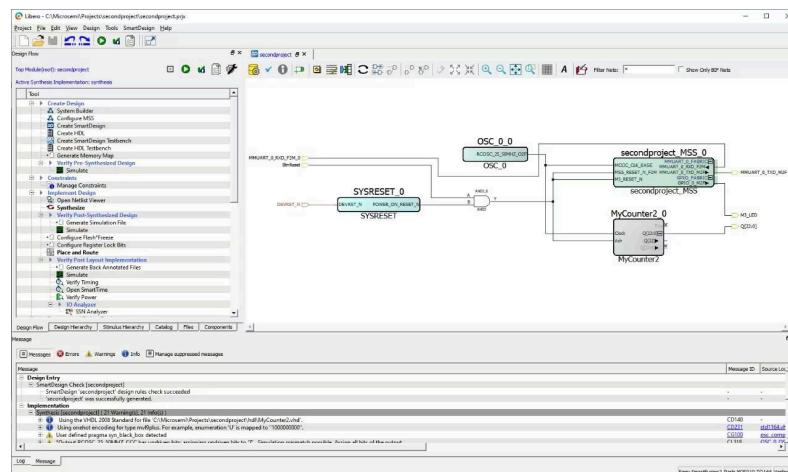


Figure 3: Microchip Libero




2.5 Cabling

Since every RC Kart is unique, you will probably use different input and output signals. This needs to be reflected in the Pin Constraint file which can be found under **Board(concat/Kart.pdc)**.




The master solution already programmed on the board for tests uses the direct connection schematic.

Hereafter two examples:

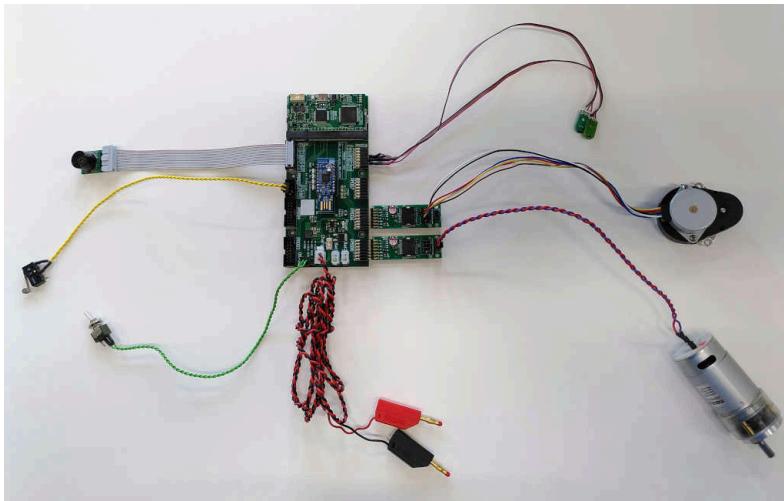

Module	Pmod Nb
Range Sensor	PM1 (8)
Stepper End	PM2 (1)
Leds out.	PM4
DC Motor	PM5 (5, 6)
Stepper Motor	PM6 (5 to 8)
Buttons in.	PM7 (5 to 8)
Hall Sensor	PM8 (4)

Figure 4: Hardware Cabling (direct connection, **Kart.pdc**)

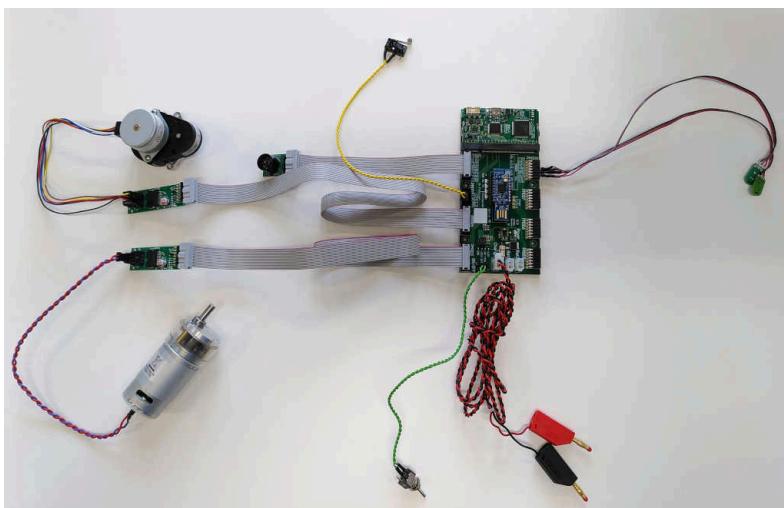

Module	Pmod Nb
Range Sensor	PM1 (8)
Stepper End	PM2 (1)
DC Motor	PM3 (5, 6)
Stepper Motor	PM4 (5 to 8)
Leds out.	PM6
Buttons in.	PM7 (5 to 8)
Hall Sensor	PM8 (4)

Figure 5: Hardware Cabling (flat cables, **Kart_FlatCables.pdc**)



3 | System Architecture

The architecture is essentially split between two parts: the embedded electronic which drives the kart and read the various sensors, communicating with a smartphone to be controlled remotely. In this section only the mandatory functions are described.

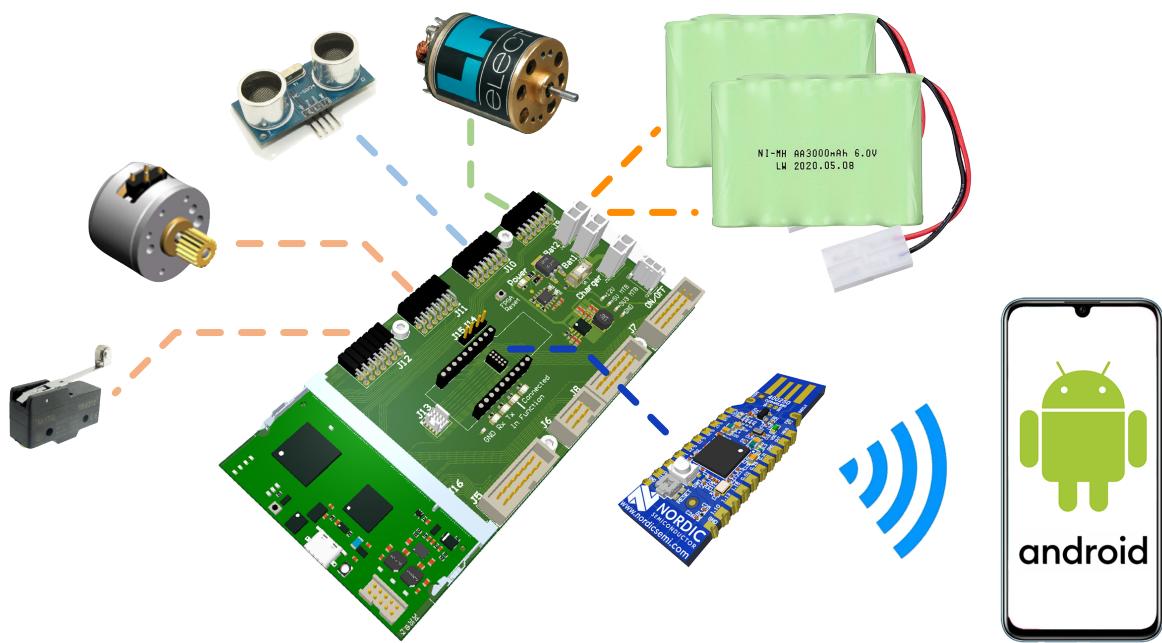


Figure 6: System Architecture Overview

(The shown config is custom and does not correspond to Figure 4 or Figure 5)

Contents

3 System Architecture	10
3.1 Block diagram	11
3.2 Functions	12



3.1 Block diagram

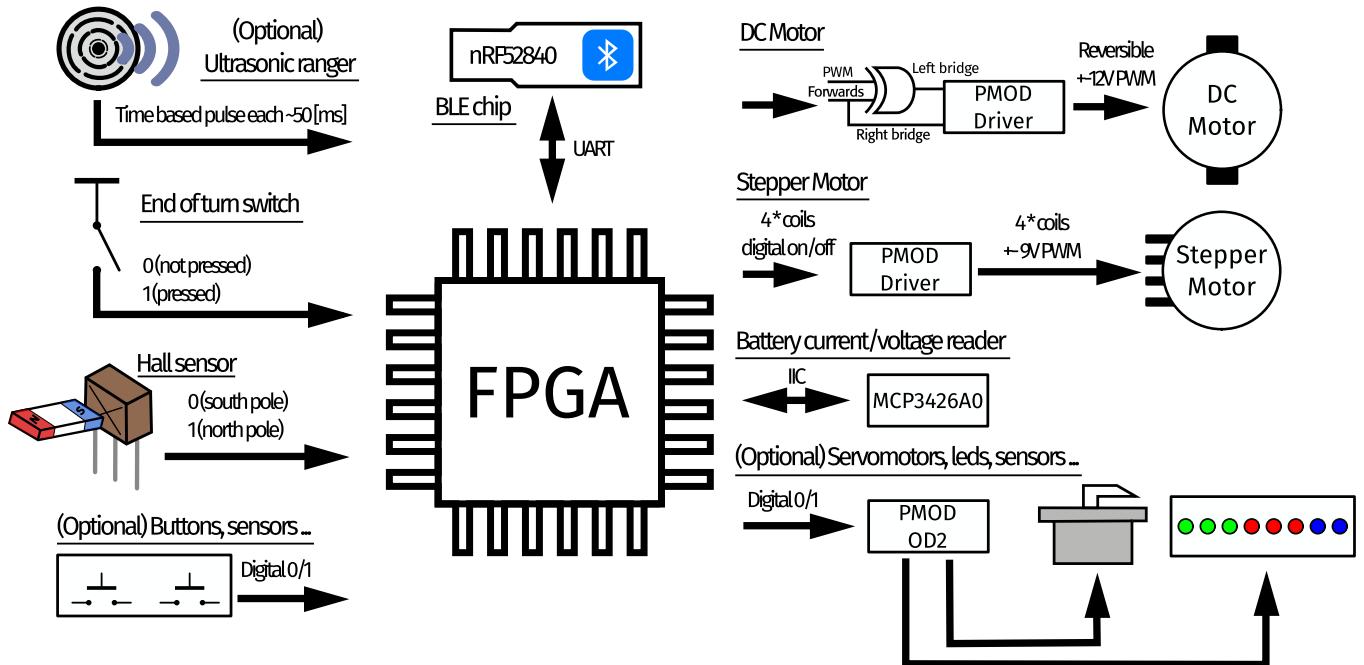


Figure 7: Electronic Architecture

The system is centered around the FPGA which gets the following inputs:

- **Ultrasonic ranger (optional)**: permits to detect distances and brake in case of an obstacle
- **End of turn switch**: used to zero the wheels angle of the Kart
- **Hall sensor**: combined to magnets, allow to calculate the car speed
- **Buttons, sensors ... (optional)**: any extra hardware which creates 0-3.3V digital inputs can be wired to the FPGA and used internally for extra features

The followings are available on the board itself:

- **User leds (optional)**: 3 user leds can be freely controlled for debug purposes
- **BLE chip**: the FPGA communicates through UART with a nRF52849 BLE chip to link with the smartphone
- **Battery reader**: a MCP3426A0 chip allow to read through I2C both the current and voltage from the system

Finally, outputs are:

- **DC motor**: the system is propelled by a 12V brushed DC motor
- **Stepper motor**: the steering of the car is carried out by a 4 coils stepper motor
- **Servomotors, leds, sensors ... (optional)**: any digital output can be wired to the FPGA through the PMOD-OD2 board. This board can translate the outputs to higher-current and voltages. The selectable output voltages of this board are +3.3, +5 or +12 V



3.2 Functions

The minimal system allows to communicate with the smartphone as well as operate all required sensors and actuators. The system needs to:

- Propel the kart forward and backward with the help of the DC motor - Section 4.4.1 - and motor driver PMOD - Section 4.4.3
- Steer the kart with the help of the stepper motor - Section 4.4.2, a motor driver PMOD board - Section 4.4.3 - and the end of turn switch - Section 4.5
- Count the hall sensor - Section 4.6 - pulses to measure the speed
- Set registers correctly to communicate through the UART serial link with a custom communication protocol - Section 7 - with the smartphone over bluetooth - Section 4.7.



4 | Hardware Components

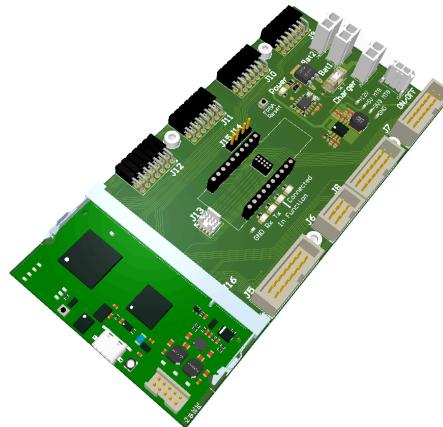


Figure 8: Kart PCB

Contents

4 Hardware Components	13
4.1 Good Practices	14
4.2 Motherboard (MB)	14
4.2.1 Power	14
4.2.1.1 Charging	14
4.2.1.2 Power-on	14
4.2.1.3 Power State	15
4.2.2 SODIMM Daughterboard Connector	15
4.2.3 I/Os	15
4.2.4 FPGA Reset	16
4.2.5 UART Sniffer	16
4.2.6 BLE Socket	16
4.3 Dautherboard (DB)	17
4.3.1 Power	17
4.3.2 Programming	17
4.3.3 Connection with Motherboard	17
4.3.4 I/O	18
4.4 Motors	19
4.4.1 DC-Motor	19
4.4.2 Stepper-Motor	19
4.4.3 PMOD DC-Stepper Control board	20
4.5 End of turn switch	21
4.6 Hall Sensor	21
4.7 Bluetooth Dongle NRF52840	22
4.8 Sensor & I/O	22
4.8.1 Servo Motor	22



4.1 Good Practices

In order not to damage the hardware, strictly follow the Section 1 - [Security Guidelines](#).

4.2 Motherboard (MB)

The Kart motherboard can receive any compatible FPGA daughterboard - Section 4.3 such as the AGLN250 [7] one used during the Kart project. The Motherboard connects all peripherals to the I/Os and powers the system at the same time [2].

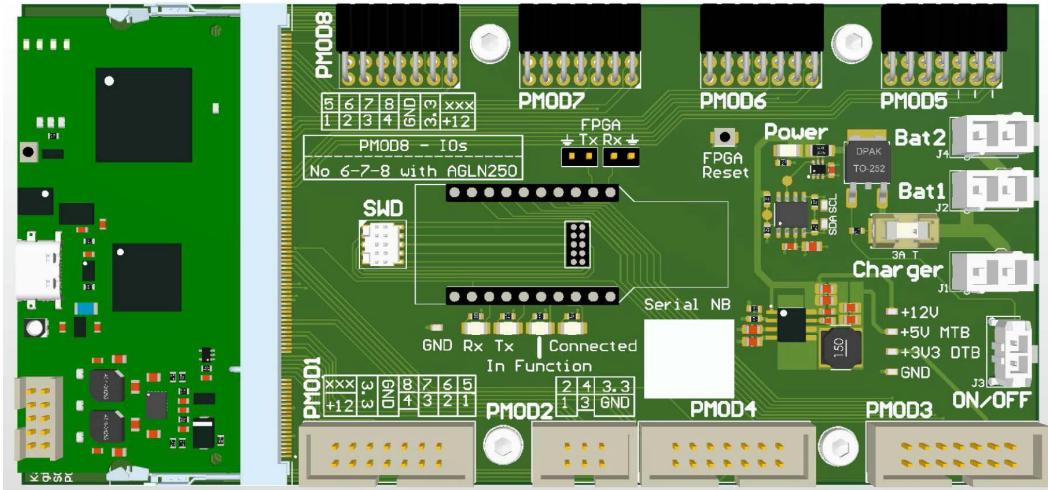


Figure 9: Motherboard PCB

4.2.1 Power

The main power entry point of the system is through the motherboard, either by using:

1. the two battery connectors with two +6V / 2400mAh packs put in series
2. the charger port with a +12V input from a regulated DC supply.

The +12V is then reduced to a +5V rail through a buck converter. Finally, the daughterboard is fed with the +5V to provide a +3.3V rail.

4.2.1.1 Charging

The Charger connector is used combined with a DC supply to test the system, but also for an NiMh charger to be connected.



Charging batteries is handled by the electronic lab directly. Simply ask and hand them your packs.

4.2.1.2 Power-on

A switch must be connected to the corresponding port to power the board. The +12V is then transported to the PMODs and the buck converter through a 1.25A-T fuse. A **green** LED shows the board power status.



Follow the tests guideline given under Section 6 before powering anything.
If the fuse breaks, check for any short-circuit before replacing it and power-cycling the circuit.

4.2.1.3 Power State

An I2C dual-inputs ADC converter (MCP3426A0) [8] is present on the board to read both the battery voltage and the current consumption.

Access the data

The chip is read from the FPGA each second through dedicated I2C lines. The information can be read from the smartphone at will by accessing the corresponding registers - Section 7.2.

4.2.2 SODIMM Daughterboard Connector

The daughterboard - Section 4.3 is connected to the motherboard through a SODIMM-200 (DDR2 RAM) connector.

4.2.3 I/Os

The board allows for multiple I/Os to be plugged following the **PMOD** wiring [9], slightly modified to add a +12V rail, under the following form:

- 4 dual connectors for direct plug (PMODs 5 to 8)
- 3 dual connectors for flat-cables (PMODs 1, 3, 4)
- 1 single connector for flat-cable (PMOD 2)



PMOD8 signals P6 to P8 cannot be used with the AGLN250 FPGA. Use only the upper row (PM8_1 to PM8_4).

The pins are described on the board itself and correspond to the following:



Figure 10: PMOD pinning (header)

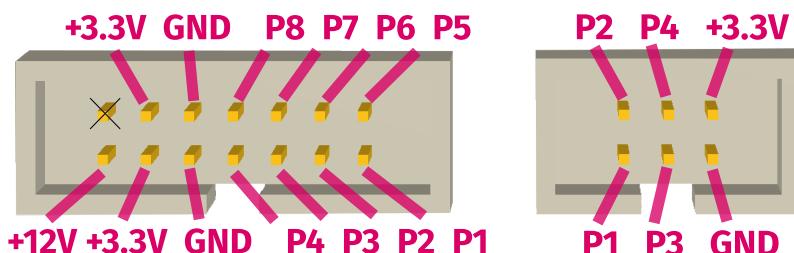


Figure 11: PMOD pinning (flat)



At all time, ensure there is **NO VOLTAGE FEEDBACK** from anything else than 3.3V on the I/Os. Use a dedicated PMOD board if needed. They are presented in the Appendix B.

4.2.4 FPGA Reset

A small button allows the user to reset the FPGA from the motherboard.

4.2.5 UART Sniffer

Both Tx from the FPGA and the BLE module can be sniffed by wiring a dedicated UART-USB chip to the provided headers or directly with an oscilloscope.

4.2.6 BLE Socket

The Bluetooth \leftrightarrow USB dongle - Section 4.7 [10] can be inserted in its dedicated socket to control the Kart with a smartphone, or easily removed to be plugged in a PC directly. One can emulate the BLE module with the help of a custom serial interpreter - Section 6.4 by simply plugging the daughterboard in a PC through the USB-C. The communication is merged between both the PC and the BLE module.



Trying to communicate simultaneously from the BLE module and the PC will result in undefined behavior (surely scrambled and wrong data read by the FPGA).

One can listen to what the FPGA communicates to the BLE module by opening a serial terminal on the USB-C COM port, but not the other way around.



4.3 Dautherboard (DB)

The FPGA daughterboard embeds an Igloo **AGLN250** chip [7] in a **VQ100** package, driven by a **10MHz** clock.

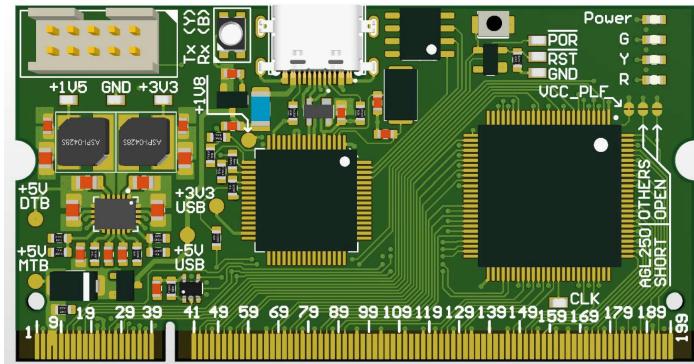


Figure 12: Daughterboard PCB

4.3.1 Power

The board is powered either through an USB-C connector (+5V, providing a JTAG access along an USB-UART converter [11]) or through the motherboard - Section 4.2 via an external +5V rail. It will automatically resolve the path if both supplies are wired simultaneously, choosing the motherboard rail in priority.

Internally, it creates a +3.3V rail used by both the FPGA and the motherboard, plus another +1.5V rail for the FPGA core supply.

4.3.2 Programming

The board can be programmed by using Libero IDE - Appendix A.3 and plugging a [Microsemi FlashPro 4](#) dongle on the dedicated 10 pins header.

It is also possible to use the USB-C connector with the help of [OpenOCD](#) and custom scripts. Both the USB and the FlashPro can be plugged at the same time. The FlashPro gains priority over the USB JTAG signals.



While using the FlashPro without the motherboard powered, it is necessary to plug both the USB-C and the FlashPro to be able to program the card.

4.3.3 Connection with Motherboard

The board is linked to the motherboard - Section 4.2 through an SODIMM-200 connector (the 200 gold fingers on the FPGA board) [2]. By design, it cannot be inserted the wrong way.

The connector pinning is shown in the Kart Pinning Datasheet [12].



4.3.4 I/O

Reset

A button is found on the board to reset the FPGA.



Be careful when pushing it while it is inserted in a motherboard. Do not apply force on the SODIMM connector.

LEDs

A **blue LED** indicates that the board is powered (top right of the board), while a second (found near the USB connector) shows in and out transaction over UART.

Red, **yellow** and **green** LEDs found under the power indicator can be freely controlled by the user.

PoR

The board also embeds a Power on Reset (PoR) circuitry that will detect low FPGA voltage and reset it (discharged batteries, too high current consumption ...).



4.4 Motors

4.4.1 DC-Motor

The DC Motor is used to propel the kart forward. It is a brushed DC motor, running on +12V and drawing a current of $I_{\max} = 0.7A$ and $I_{\text{idle}} = 0.32A$ [1]. The PMOD DC-Stepper Motor Driver allows to control the motor via a [PWM Signal](#) [13] through a [H-Bridge](#) [14].



Figure 13: Modelcraft RB350018-2A723R DC Motor and its pinning

4.4.2 Stepper-Motor

The Stepper Motor is used for steering the kart. It is a bipolar stepper motor with a step angle of 7.5° - 48 steps per rotation and a nominal current of $I = 0.86A@5V$ with a $R = 5.8\Omega$ [15]. It is attached to a 100:1 reductor gear which leads to an output axis with a step angle 0.075° - 4800 steps per rotation.

The motor is controlled with the PMOD DC-Stepper Motor Driver - Section 4.4.3 hosting a dual full [H-Bridge](#) to control the 4 coils of the stepper motor.

The calibration can be performed using the End-of-Turn switch - Section 4.5.

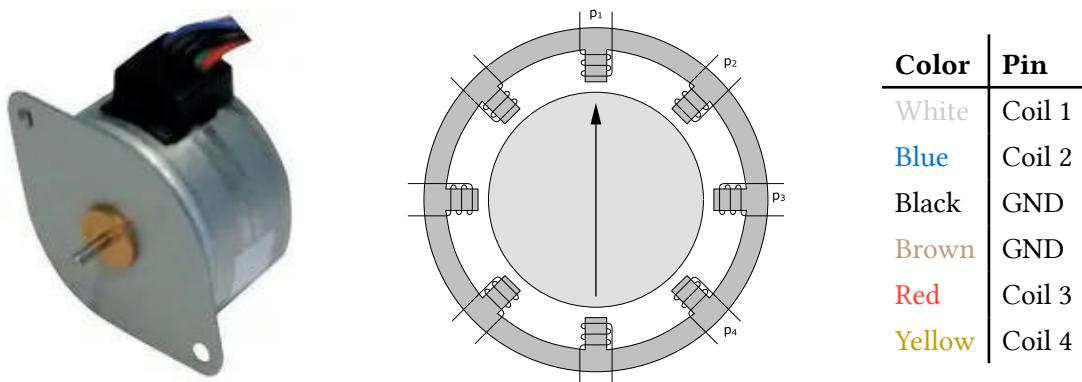


Figure 14: Nanotec SP3575M0906-A Steppermotor, coils and pinning




4.4.3 PMOD DC-Stepper Control board

The control board hosts a dual full [H-Bridge](#) and a circuitry to create the switching dead-times [16]. It allows to control both the DC motor or the stepper motor.

The 6-pins connector is used to connect a stepper motor and the 2-pins one the DC Motor.



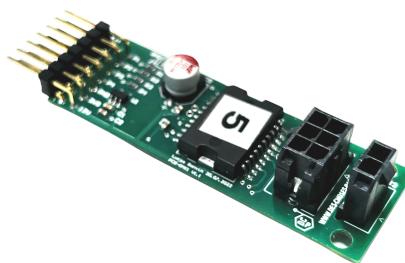Only one motor can be connected at any given time.



Row	Pin	Descr.	Row	Pin	Descr.
Top	2	P1 NC	Bottom	1	P5 In Left Bridge A
	4	P2 NC		3	P6 In Right Bridge A
	6	P3 NC		5	P7 In Left Bridge B
	8	P4 NC		7	P8 In Right Bridge B
	10	GND		9	GND
	12	3.3V		11	3.3V
	14	12V		13	NC

Figure 15: PMOD DC-Stepper Control board and pinning

The Figure 16 shows the bloc diagram of the main component, the L298P:

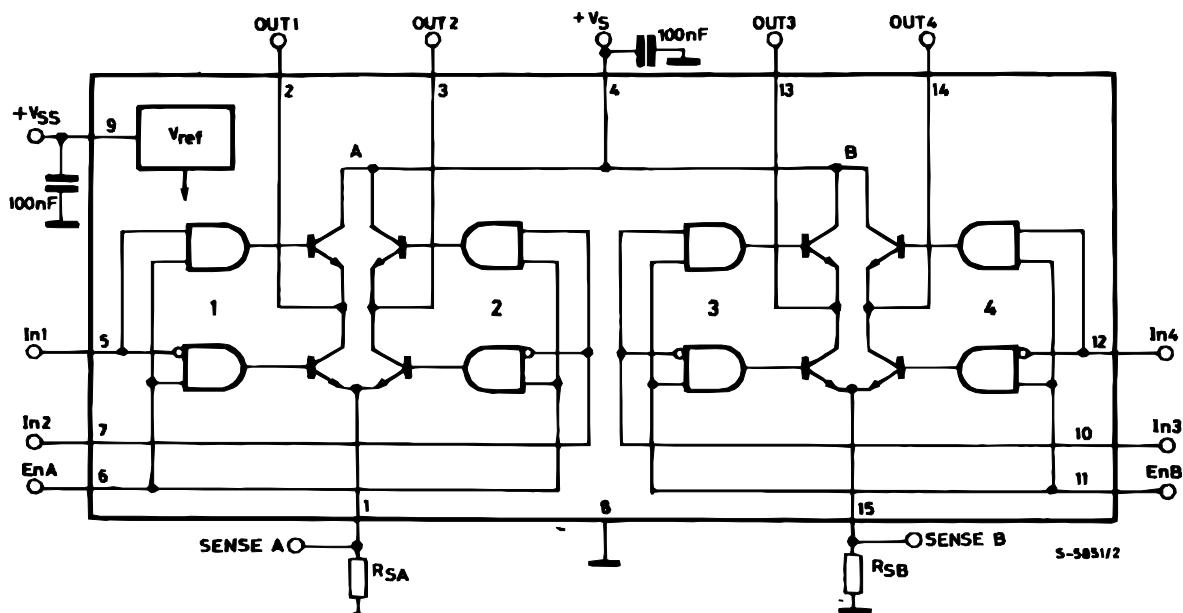


Figure 16: PMOD DC-Stepper Control board



4.5 End of turn switch

The end of turn switch can be plugged into any PMOD connector and is used to identify the steering “zero” position. The used switch is a Omron miniature high reliability and security switch [17].

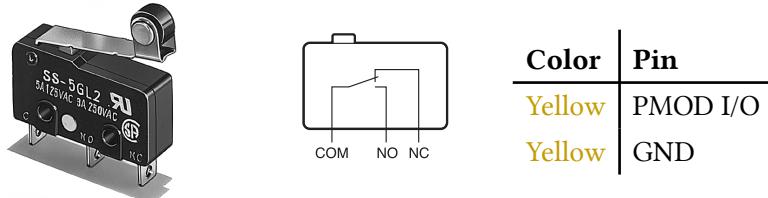


Figure 17: Omron SS-5T Miniature High Reliability and Security Switch and its pinning



An internal pull-up must be enabled on the FPGA side.

4.6 Hall Sensor

One or two Hall sensors are used to track the distance driven by the kart. The SS311PT/SS411P digital Hall-effect sensors [18] are operated by a magnetic field and designed to respond to **alternating** North and South poles with their **Schmitt-trigger** [19] output.

They can be powered between **2.7Vdc** to **7Vdc** with an open collector output integrating a $10\text{k}\Omega$ pull-up resistor already.



Figure 18: Hall Sensor Honeywell SS311PT and its wiring



No internal pull resistor should be enabled on the FPGA side.



4.7 Bluetooth Dongle NRF52840

The nRF52840 Dongle is a small, low-cost USB dongle that supports Bluetooth 5.4, Bluetooth mesh, Thread, Zigbee, 802.15.4, ANT and 2.4 GHz proprietary protocols [10], [20]. In this project it is used to communicate with the smartphone. The output of the dongle is an UART serial link that is connected to the FPGA. The communication protocol is defined in Section 7.



Figure 19: NRF52840 Bluetooth Dongle

4.8 Sensor & I/O

Various sensors can be mounted on the motherboard - Section 4.2 through the exposed PMOD - Appendix B connectors.

Any +3.3V I/O which consumes less than 8 mA can be connected on any PMOD connector (either by directly plugging them into the pin headers or through the IDC cables).

Only **pins 6, 7 and 8 of the PMOD8 CANNOT be used** with the current FPGA.

4.8.1 Servo Motor

Servos are a great choice for robotics projects, automation, RC models and so on. They can be used to drive custom mechanical parts of your RC-Car. The angle is controlled with the control pin. The pulse width of a $f = 50\text{Hz}$ signal defines the angle, see Figure 20.

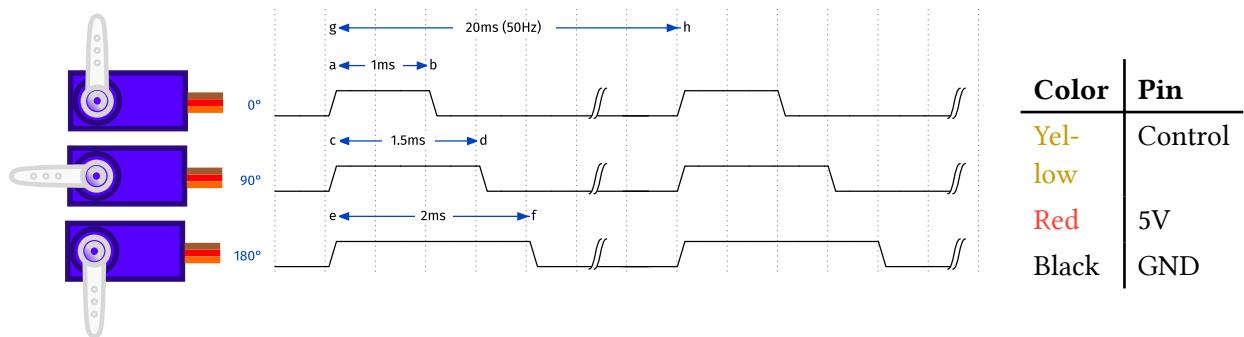


Figure 20: Servo Motor Control and pinning

Use boards like the PMOD-OD2 - Appendix B.2.1 to control such devices.



5 | FPGA Design

At least the three different modules must be completed:

- The DC motor controller (Section 5.1) receives a **prescaler** and a **speed value** to build the corresponding PWM and **direction** signals.
- The stepper motor controller (Section 5.2) receives a **prescaler** and the desired **angle** and builds the **coil** controls signals.
- The sensor controller (Section 5.3) manages I/O comprising the **hall sensors** to retrieve the driving speed and the **range finder** to get the distance from an obstacle (optional).

Contents

5 FPGA Design	23
5.1 DC Motor Controller	24
5.1.1 Functionality	24
5.1.1.1 PWM Generation	25
5.1.1.2 Hardware orientation	25
5.1.2 Bluetooth connection	25
5.1.3 Tests	25
5.2 Stepper Motor Controller	26
5.2.1 Functionality	26
5.2.2 Driving coils	26
5.2.3 Zero position	27
5.2.4 Hardware orientation	27
5.2.5 Initial position	28
5.2.6 Tests	28
5.3 Sensors Controller	29
5.3.1 Functionality	29
5.3.2 Hall counter	30
5.3.2.1 Tests	30
5.3.3 Ultrasound Ranger (<i>Optional</i>)	31
5.3.3.1 Tests	31



5.1 DC Motor Controller

The DC motor controller is in charge of the Kart's propulsion, both in forward and reverse.

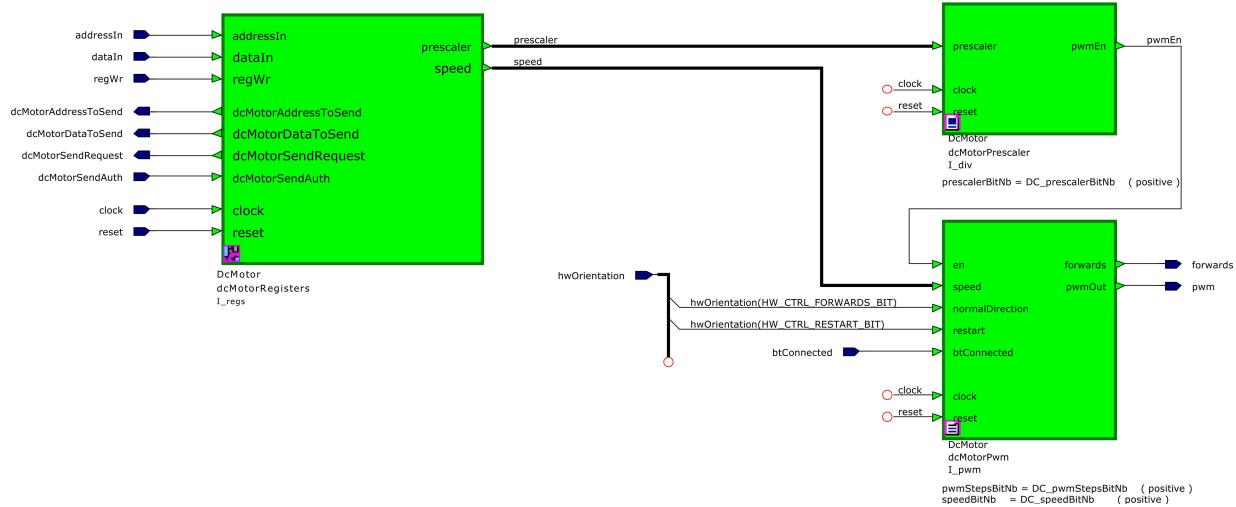


Figure 21: DC module top-level

For this, two signals are generated :

- A **pwm** with a controllable frequency whose duty-cycle is modified to control the speed
- A **forwards** signal to drive either forward or backward.

The speed is set in the DC motor speed register - Section 7.2, ranging from **-15=0b1001** to **15=0b0111**.

The frequency is given by the **prescaler** in the DC motor prescaler register - Section 7.2 following the formula:

$$f_{\text{PWM_DC}} = \frac{f_{\text{clk}}}{\text{PWM}_{\text{steps}} * \text{prescaler}} = \frac{10\text{MHz}}{16 * \text{prescaler}} \quad (1)$$

The minimal value of the PWM signal is studied in another part of the project.

5.1.1 Functionality

The **dcMotorPwm** block receives the **speed** signed number and has to drive the DC motor with the **pwm** and **forwards** signals. These are then converted to two driving signals controlling a [H-Bridge](#) [14].

The mean amplitude of the DC motor's voltage is set by a **PWM**:

- The **forwards** signal is derived from the sign of the **speed** control.
- The **pwm** signal is derived from the absolute value of **speed**.



The PWM signal is implemented with the help of a free-running counter and a comparator. Since the power transistors cannot switch at too high frequencies, the PWM period must be controlled.

This is achieved with the help of an **en** (enable) signal generated by the **dcMotorPrescaler** block, dividing the clock frequency. The **dcMotorPwm** counter must only increment when this signal is **en='1'**.



5.1.1.1 PWM Generation

Create a structure which is able to generate the PWM on 16 steps, cadenced by the **en** signal and whose duty is set by the absolute value of the **speed[MSB-1 : 0]** signal.

Set the **fowards** signal '**1**' if the Kart should drive forward, '**0**' otherwise.



Draw the circuit of the **dcMotorPwm** block.

5.1.1.2 Hardware orientation

The mechanical design can either lead the Kart to drive forward or backward when a positive voltage is applied to the DC motor.

In order to cope with this, a setup signal, **normalDirection**, is provided to the block. **normalDirection = '1'** means that a positive voltage applied to the DC motor lets the kart drive forwards.



Update the circuit in order to cope for the different mechanical design possibilities.

The setup bit is configured in the hardware control register - Section 7.2.

5.1.2 Bluetooth connection

When the Bluetooth connection is lost, the DC motor should not turn to prevent any damage.

A control signal, **btConnected**, is provided to the block. When **btConnected = '0'**, the DC motor must stop.

If the **btConnected** then rises back to '**1**', the motor must not move until the speed register is modified. Else the Kart would dangerously resume moving without the user being ready.

The BT connection bit is given by the hardware control register - Section 7.2.



Update the circuit in order to stop the motor on connection loss and resume only after the connection is resumed AND the speed modified.

5.1.3 Tests



Refer to Section 6.1.1 - [DC Motor testing](#) to test your block fully before deploying it on the FPGA.



5.2 Stepper Motor Controller

The stepper motor controller is in charge of the Kart's steering to reach the desired angle. For this, four signals are generated to control the four coils of the motor:

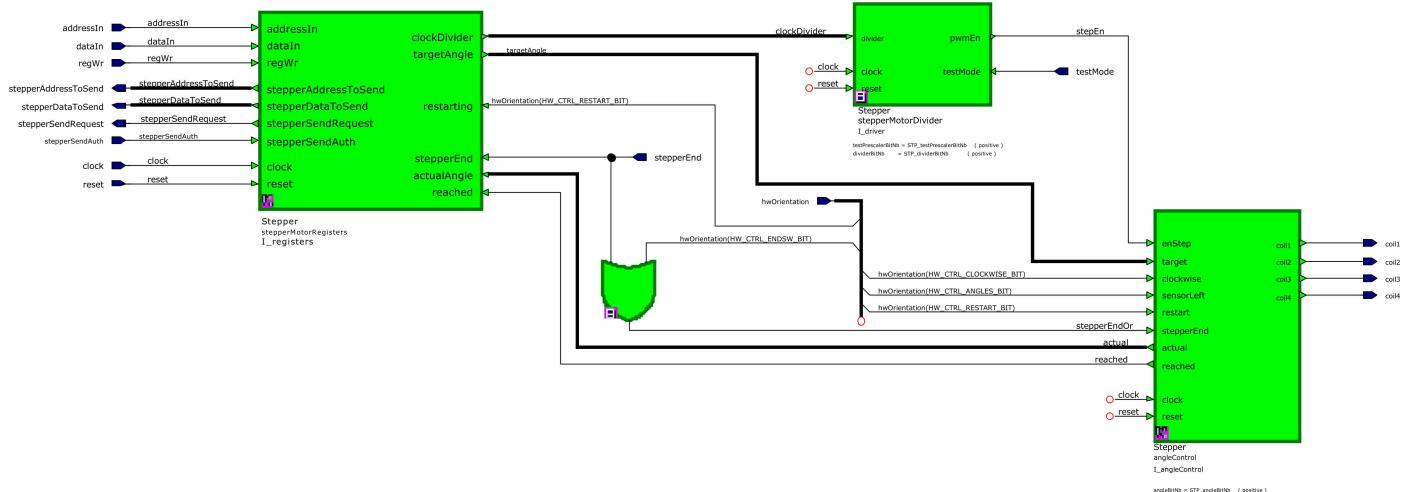


Figure 22: Stepper module top-level

The **angleControl** block is in charge to generate the 4 phases to turn the kart's steering wheels to the desired angle.

The unsigned signal **targetAngle** is set in the stepper motor target angle register - Section 7.2 and the current angle written to the **actualAngle** register.

The frequency is given by the **prescaler** register following the formula:

$$f_{\text{PWM_step}} = \frac{f_{\text{base}}}{\text{prescaler}} = \frac{100\text{kHz}}{\text{prescaler}} \quad (2)$$

Too high frequencies will result in the motor tripping or slipping.

5.2.1 Functionality

The **angleControl** block receives a **targetAngle** and has to step the coils at each occurrence of the **enStep** signal until the desired angle is reached. This signal is generated by the **stepperMotorDivider** block.

The coils are controlled through the 4 outputs **coil1** to **coil4**. When a '1' is applied, the corresponding coil draws current and becomes magnetized.

The taken steps are updated live on the **actual** vector to reflect the current Kart's steering and the flag **reached** set to '1' when the requested position is reached. The information is then automatically sent to the smartphone.



The angle values represent the number of steps of the steppermotor. The maximum angle is 360°, which corresponds to 4800 steps see Section 4.4.2

5.2.2 Driving coils

To control the stepper, one coil at a time should be magnetized, known as **wave drive**.



Other driving methods such as full-step, half-step and microstepping are further ideas which can be counted as extra features for your Kart, as well as reducing the current consumption with some PWM s.

Each time the signal **stepEn** is '**1**', the coils must change state as long as the current angle has not reached the target. For that, a counter must remember how many steps have been taken until now and write it in the vector **actual**.

Keep the flag **reached** to '**0**' as long as the target is not reached, else indicate it with a '**1**'. At this moment, cut off all coils to limit the current consumption. Failing to do so will result in overheating motors.

Finally, ensure that both the first and last pulse of the coils (from resuming the movement to ending it when the target is reached) have the same duration as all the others. Otherwise, the motor will not be correctly magnetized and trip.



The vector **actual** and the flag **reached** are both used internally to trigger events which will transmit their values to the smartphone. A mishandling of those signals will result in a flood of the communication system, which may in turn imply loss of data with the smartphone, commands not updating and the GUI freezing because of too many interrupts.



Draw the circuit of the **angleControl** block.

5.2.3 Zero position

The signal **stepperEnd** is linked to the mechanical switch mounted on the Kart which indicates when the steering is at 0.

When this signal rises, the **actual** vector should be reset to 0.

With this, the steering motor will not try to turn further than what the kart's mechanical structure allows it to do in one of the directions. In the other direction, it is the programmer's task not to request a too large **target** angle. This also means that the angles are always considered as positive numbers, the zero position being given by the **stepperEnd** switch.



Update the circuit to integrate the reset based on **stepperEnd**.

5.2.4 Hardware orientation

The mechanical design allows for the following variations:

- the **stepperEnd** switch can be placed such as to detect the maximal steering angle either on the left or on the right side
- switching the coil controls in the sequence $1 \Rightarrow 2 \Rightarrow 3 \Rightarrow 4 \Rightarrow 1 \Rightarrow 2 \Rightarrow \dots$ can result in the kart to turn either to the left or to the right

In order to cope with all possibilities, 2 setup signals are provided to the block:



- **sensorLeft** being '1' means that the **stepperEnd** switch is placed on the left side
- **clockwise** being '1' means that the sequence $1 \Rightarrow 2 \Rightarrow 3 \Rightarrow 4 \Rightarrow 1 \Rightarrow 2 \Rightarrow \dots$ lets the steering turn to the right

The corresponding setup bits are configured in the hardware control register - Section 7.2.



Update the circuit of the **angleControl** block in order to cope for the different mechanical design possibilities.

5.2.5 Initial position

The hardware control register - Section 7.2 also contains the bit **restart** indicating that the stepper motor has to turn all the way back until reaching the **stepperEnd**.

This bit is set by the remote control smartphone after a successful Bluetooth pairing, together with the appropriate **sensorLeft** and **clockwise** setup bits, in order for the FPGA hardware to discover the zero angle position. This should only be done after the stepper motor period register has been set to a proper value.

Resetting to the zero position can also prove beneficial in the event of excessive current draw from the batteries, leading to a power dip in the FPGA that triggers a reset.

The **restart** signal remains in a high state until either the **stepperEnd** button is pressed or it is reset by the smartphone.

- Consequently, upon detecting a restart, the system needs to transition into a restart state and proceed until the **stepperEnd** button is pressed.
- If the **restart** signal falls while the **stepperEnd** has still not been pressed, the restart must continue.
- If the switch is already pressed when **restart** rises, it stays on for only one clock period.

The stepper motor must wait for the **restart** signal to be released before acting normally. Also, it should not turn while a first **restart** has not been performed.



Update the circuit of the **angleControl** block in order to turn all the way to the **stepperEnd** position once the **restart** signal is set.

5.2.6 Tests



Refer to Section 6.1.2 - [Stepper Motor testing](#) to test your block fully before deploying it on the FPGA.



5.3 Sensors Controller

The sensors controller handles the other I/Os of the system:

- Generic, 0-3.3V digital inputs. *Up to 16 inputs.*
- Generic, 0-3.3V digital outputs. *8 available outputs.*
- Dedicated I2C battery voltage and current reader.
- Dedicated hall sensors reader.
- Dedicated supersonic range finder pulse reader.

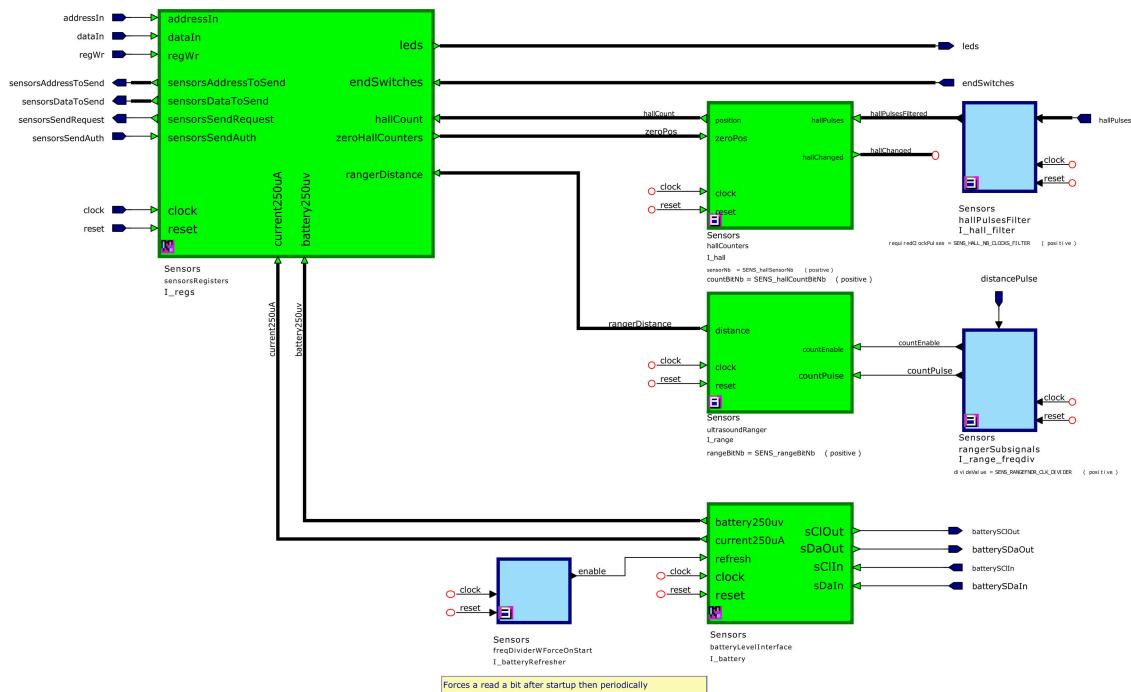


Figure 23: Sensors module top-level

5.3.1 Functionality

The **leds** vector is controlled by the smartphone and used for generic outputs at will. It can simply set those on or off, but also handle toggling them at predefined frequencies. See the LEDx registers - Section 7.2.

The **endSwitches** vector is used as generic inputs. Each transition of their value is forwarded to the smartphone.



As the state changes of the **endSwitches** are transmitted to the smartphone, these inputs are not designed for rapid fluctuations. Swift changes could potentially overwhelm the communication system, leading to issues such as data loss with the smartphone, commands failing to update, and the graphical user interface (GUI) freezing due to an excessive number of interrupts.

The **freqDividerWForceOnStart** along the **batteryLevelInterface** blocks handle communication with the motherboard's I2C voltage and current reader - see Section 4.2.1.3. Both values are read periodically, typically each second, and forwarded to the smartphone when they change from at least a predetermined value.



5.3.2 Hall counter

The hall sensors presented in Section 4.6 create pulses based on the speed of the Kart. They are first passing through the **hallPulsesFilter** block which is implemented and does the following:

- Get the raw pulses from the hall sensors
- Debounces the input to avoid false transitions
- Transmits the filtered pulses to the **hallCounters** block

The **hallPulses** vector contains one signal per hall pulse sensor.

Even if you only use one hall sensor, the second exists, just held to '0' at all time.

The following behavior must be implemented:

- The **hallCounters** block receives the **hallPulses** vector and has to count the number of pulses for each sensor.
- If the vector **zeroPos** is set to '**1**' for a particular sensor, the corresponding **hallCount** value is reset. Subsequently, if the zeroPos vector is '**0**', the dedicated counter should be incremented either on:
 - The rising edge of the pulse
 - Both the rising and falling edges of the pulse



The final determination of counting behavior depends on the desired functionality for your Kart. If you prefer counting on both edges for better precision, set the corresponding value in the **Kart/Kart_Student** package. Adjust the variable **HALLSENS_2PULSES_PER_TURN** to '**1**' if the signal is counted on each edge, or '**0**' if counted only on one edge.

*The signal **hallChanged** is currently unused.*

The two hall counters values must be concatenated to the **hallCount** vector. The second counter needs to be shifted by 16bit: $\text{hallCount} = (\text{hallCount}_2 \ll 16) + \text{hallCount}_1$. It must **AT ALL TIME** reflect the current counters values.



Draw the circuit of the **hallCounters** block.

5.3.2.1 Tests



Refer to Section 6.1.3 - [Sensors testing](#) to test your block fully before deploying it on the FPGA.



5.3.3 Ultrasound Ranger (*Optional*)

An ultrasound ranger is useful to detect obstacles in the front or back of the Kart. Based on the [PMOD-MAXSONAR](#) board from Digilent, it can be plugged into any one-row PMOD connector.



beware not to wire it on the +12V pin !

The ranger outputs a pulse named **PW** whose length is to be counted. The distance to an object is then determined following the rule $147 \frac{\mu s}{\text{inch}} = 57.84 \frac{\mu s}{\text{cm}}$.

There is no start/stop indication: the sensor continuously outputs pulses between 0.88 and 37.5 ms long, each 49 ms.

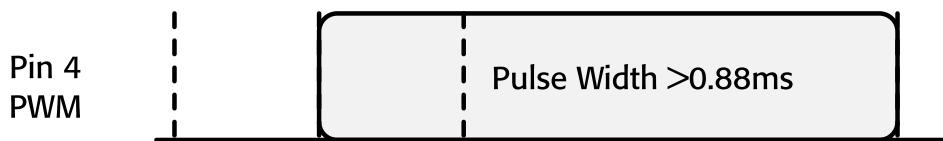


Figure 24: MaxSonar PW pulse

The pulse first goes through the **rangerSubsignals** block which does the following:

- Gets the raw **distancePulse** signal, continuously coming in as the sensor is configured to always take measurements
- Around each 333 ms, it waits for a fresh measurement, i.e. **distancePulse** falling then rising again
- The **countEnable** signal will then rise to indicate that **countPulse** must be counted
- **countPulse** creates a pulse every 1 us, as counting the clock directly is impossible since an overflow of the register may occur
- **countEnable** finally falls at the end of the measurement

So the block **ultrasoundRanger** must implement the following behavior:

- Wait for the signal **countEnable** to be '**1**'
- Count the pulses from **countPulse** as long as **countEnable** is '**1**'
- When it goes back to '**0**', the counter value must be output to the **distance** signal



The signal **distance** must be updated only when **reset = '1'** or when **countPulse** falls, the signal being kept intact until the next measurement is completed.



Draw the circuit of the **ultrasoundRanger** block.

5.3.3.1 Tests



Refer to Section 6.1.3 - [Sensors testing](#) to test your block fully before deploying it on the FPGA.



6 | Testing

Three types of testers are available to fully validate the design before flashing the FPGA.

Per module simulation - specific functionalities of the circuit:

- DC Motor Module - Section 6.1.1
- Stepper Motor Module - Section 6.1.2
- Sensors Module - Section 6.1.3

Circuit simulation - overall circuit behavior:

- Overall circuit (modules only) - Section 6.2.1
- Full circuit (with COM emulation) - Section 6.2.2

Finally, a USB tester - Section 6.4 allows to test and control the Kart by using a PC to emulate the smartphone by connecting it directly via USB.



Always complete simulations tests before any wiring and programming of the board. Always use a stabilised DC power supply while developing.

Contents

6 Testing	32
6.1 Per module	33
6.1.1 DC Motor testing	33
6.1.1.1 Testing	33
6.1.2 Stepper Motor testing	35
6.1.2.1 Testing	35
6.1.3 Sensors Controller testing	37
6.1.3.1 Testing	37
6.2 Whole circuit	38
6.2.1 Modules Simulation	38
6.2.1.1 Tests	40
6.2.2 Full-board	40
6.3 Programming the board	40
6.4 USB commands emulation	41
6.4.1 Quick Test	41
6.4.2 Registers R/W	42



6.1 Per module

Each module can be tested individually.

6.1.1 DC Motor testing

The DC motor functionality can be tested through the **DCMotor_test** \Rightarrow **dcMotorController_tb** block.

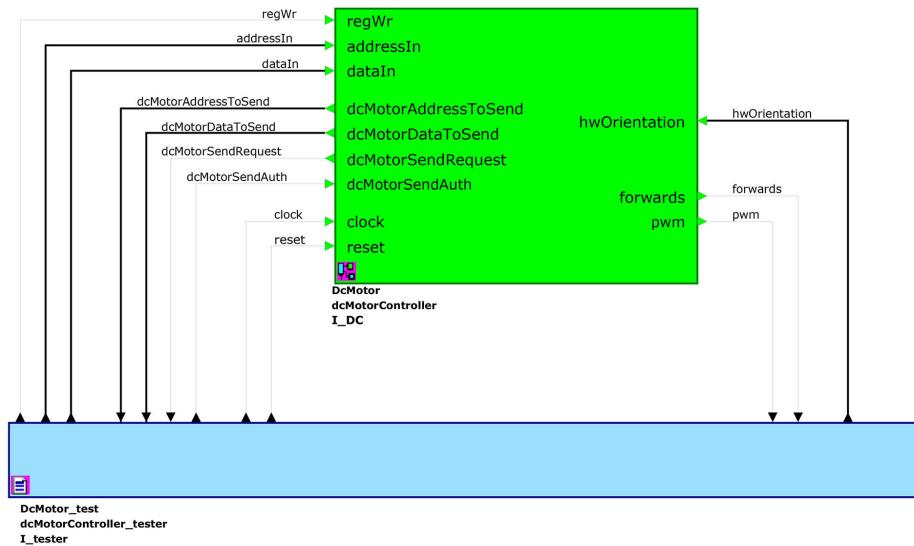


Figure 25: DC Module Testbench

The corresponding simulation layout file for Modelsim is available under **\$SIMULATION_DIR/ DCMotor/dcMotorController.do**. It will automatically run the simulation if it has not been modified.

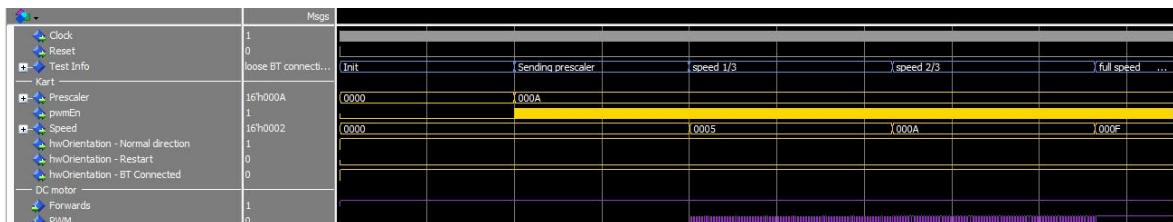


Figure 26: DC Module Simulation

- The **blue** header shows which test is performed
- The **yellow** signals are those generated by the tester
- The **purple** signals are the one generated by your implementation

6.1.1.1 Testing

The following tests are performed:

- The **prescaler** signal is set to **10**
- Positive speeds of **33%**, **66%** and **100%** are tested, expecting a correct **PWM** period and **forwards = '1'**
- Negative speeds of **33%**, **66%** and **100%** are tested, expecting a correct **PWM** period and **forwards = '0'**



- The **normalDirection** is inverted
- Positive speeds of **50%** and **100%** are tested, expecting a correct **PWM** period and **forwards = '0'**
- Negative speeds of **50%** and **100%** are tested, expecting a correct **PWM** period and **forwards = '1'**
- **Restart** is held at '**1**' while **normalDirection** is inverted again, expecting **PWM = '0'** and **forwards = '1'**
- **Restart** is released, expecting correct **PWM** and **forwards = '1'**
- The **btConnected** is lost, expecting **PWM = '0'**
- The **btConnected** is retrieved, expecting **PWM = '0'** (by security, the Kart should not restart until receiving a new **speed** command)
- A **speed** of **0** is set, expecting **PWM = '0'** and **forwards = '1'** (in the real world, it is automatically done by the smartphone once reconnected)
- A **speed** of **50%** is set, expecting a correct **PWM** period and **forwards = '1'**

Transcript

The transcript window gives you details on if tests passed or not:

- For the **PWM** signal, you get **PWM OK** or **PWM Error**.
- For the **forwards** signal, you get **Direction OK** or **Direction Error**.



6.1.2 Stepper Motor testing

The stepper motor functionality can be tested through the **StepperMotor_test** ⇒ **stepperMotorController_tb** block.

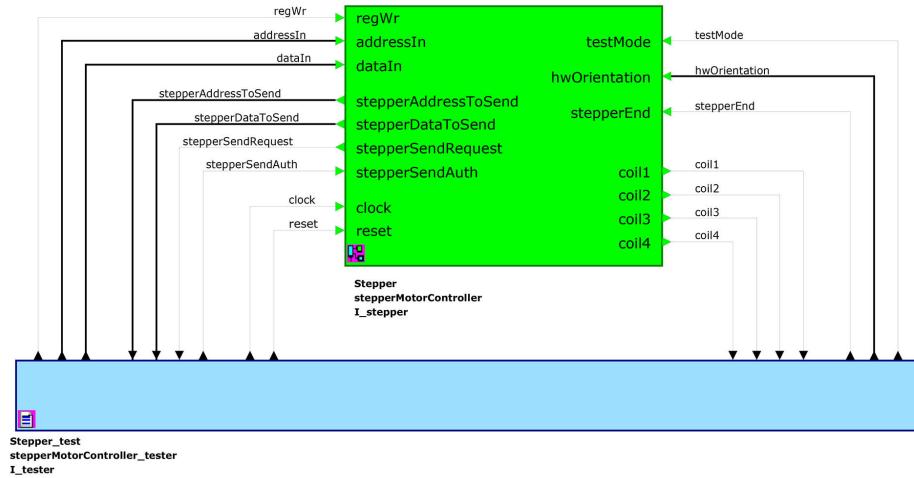


Figure 27: Stepper Module Testbench

The corresponding simulation layout file for Modelsim is available under **\$SIMULATION_DIR/Stepper/stepperMotorController.do**. It will automatically run the simulation if it has not been modified.

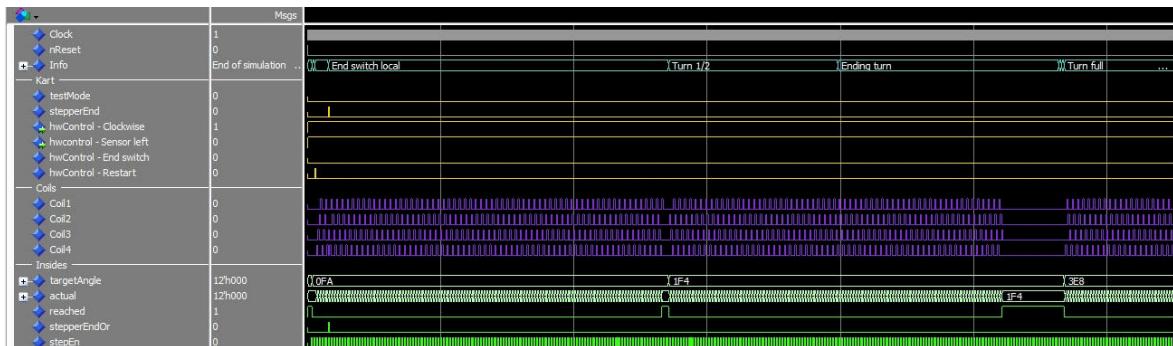


Figure 28: Stepper Module Simulation

- The **blue** header shows which test is performed
- The **yellow** signals are those generated by the tester
- The **purple** signals are the one generated by your implementation
- The **green** signals are internal ones

6.1.2.1 Testing

The following tests are performed :

- The **prescaler** is set, outputting pulses on **stepEn**
- The **restart** signal pulses (both one pulse or constant '1' are valid), expecting the coils to turn as $4 \Rightarrow 3 \Rightarrow 2 \Rightarrow 1 \Rightarrow 4 \dots$
- The **restart** signal is released, expecting the coils to keep turning
- The **stepperEnd** is pressed, expecting the coils to stop
- A **target** of **250** is set, expecting the coils to move in order $1 \Rightarrow 2 \Rightarrow 3 \Rightarrow 4 \Rightarrow 1 \dots$
- The **reached** signal should be '1' when **250** pulses have been made



- A **target** of **500** is set, expecting same behavior as before
- The **target** suddenly changes back to **0**, expecting the coils to move in the reversed sequence of $4 \Rightarrow 3 \Rightarrow 2 \Rightarrow 1 \Rightarrow 4\dots$
- The **reached** signal should be '**1**' when **actual** reaches **0**
- A **target** of **250** is set
- A new **restart** is issued as before, while the sensor left signal is set to '**0**', expecting the coils to turn as $1 \Rightarrow 2 \Rightarrow 3 \Rightarrow 4 \Rightarrow 1\dots$
- A **target** of **250** is set, expecting the coils to move in order $4 \Rightarrow 3 \Rightarrow 2 \Rightarrow 1 \Rightarrow 4\dots$
- The **reached** signal should be '**1**' when **250** pulses have been made
- A **target** of **0** is set, expecting the coils to move as $1 \Rightarrow 2 \Rightarrow 3 \Rightarrow 4 \Rightarrow 1\dots$
- The **reached** signal should be '**1**' when **actual** reaches **0**
- A new **restart** is issued as in the beginning after trying to reach a **target** of **500**, expecting the coils to turn as $4 \Rightarrow 3 \Rightarrow 2 \Rightarrow 1 \Rightarrow 4\dots$
- The **hwControl - end switch** (emulated **stepperEnd**) is pressed, expecting the coils to stop

Transcript

The transcript window gives you details on if tests passed or not:

- For the **Coil1...4** signals, you get **Coil direction OK** or **Coil direction error**.
- For the **reached** signal, you get **Reached flag OK** or **Reached flag error**.
- For the **actual** signal, you get **Position readback OK** or **Position readback error**.



6.1.3 Sensors Controller testing

The Hall Sensor and Ultrasound Ranger can be tested through the **Sensors_test** \Rightarrow **sensors_tb** block.

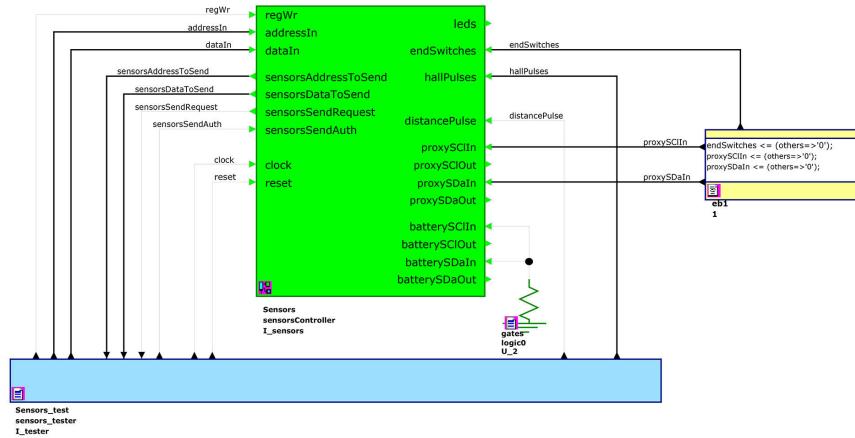


Figure 29: Sensors Module Testbench

The corresponding simulation layout file for Modelsim is available under **\$SIMULATION_DIR/Sensors/sensors.do**. It will automatically run the simulation if it has not been modified.

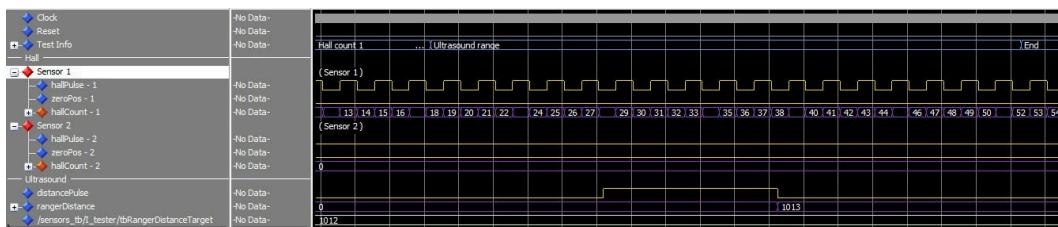


Figure 30: Sensors Module Simulation

- The blue header shows which test is performed
- The yellow signals are those generated by the tester
- The purple signals are the one generated by your implementation
- The green signals are internal ones

6.1.3.1 Testing

The following tests are performed for the Hall sensors:

- For each sensor, a pulse of a fixed period (n times slower for each new sensor) is generated
- The **hallCount** is compared to an internal counter, depending on the **HALLSENS_2PULSES_PER_TURN** constant
- When **zeroPos** goes to '1', the **hallCount** should be reset

The following tests are performed for the Ranger:

- A pulse of $\text{tbRangerDistanceTarget}(1012) * \left(\frac{T_{\text{clk}}}{10}\right)$ is generated
- When the signal **distancePulse** falls, the **rangerDistance** should be a value within 1011 to 1013

Transcript

The transcript window gives you details on if tests passed or not:

- For the **hallCount** signal, you get **Hall count n OK** or **Hall count n error**.
- For the **rangerdistance** signal, you get **Ultrasound ranger OK** or **Ultrasound ranger error**.



6.2 Whole circuit

6.2.1 Modules Simulation

In addition to the dedicated modules testers, the overall behavior can be tested through the **Kart_test** \Rightarrow **kartController_tb** block.

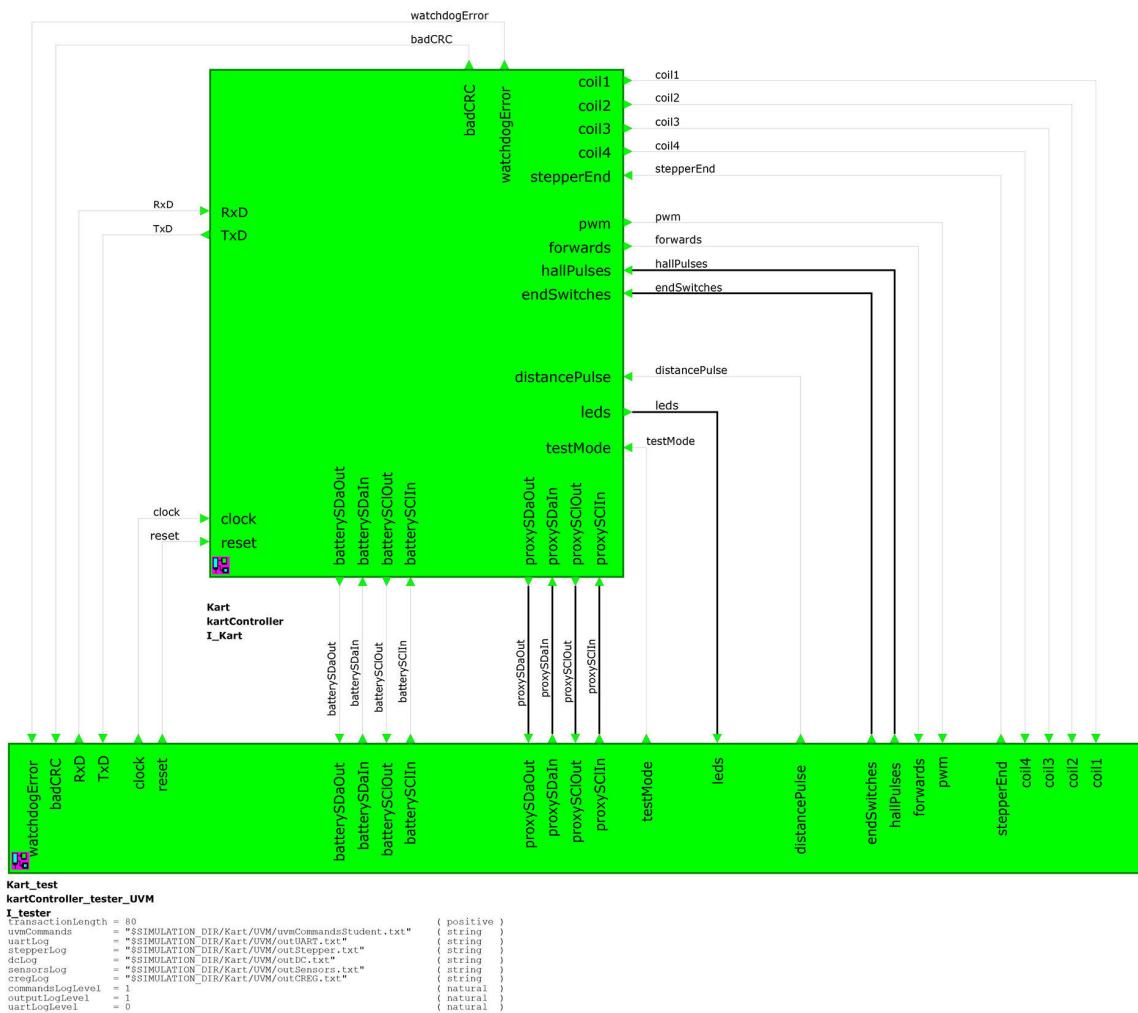


Figure 31: Kart Toplevel Testbench

The tester internal layout differs because it makes use of the UVM technology - see Figure 32.

The tester reads the commands given in **\$SIMULATION_DIR/Kart/UVM/uvmCommandsStudent.txt** and creates different logs under **\$SIMULATION_DIR/Kart/UVM/outXXX.txt**. The file can be modified without the circuit being recompiled. The corresponding simulation layout file for Modelsim is available under **\$SIMULATION_DIR/Kart/kartStudent.do**. It will automatically run the simulation if it has not been modified.

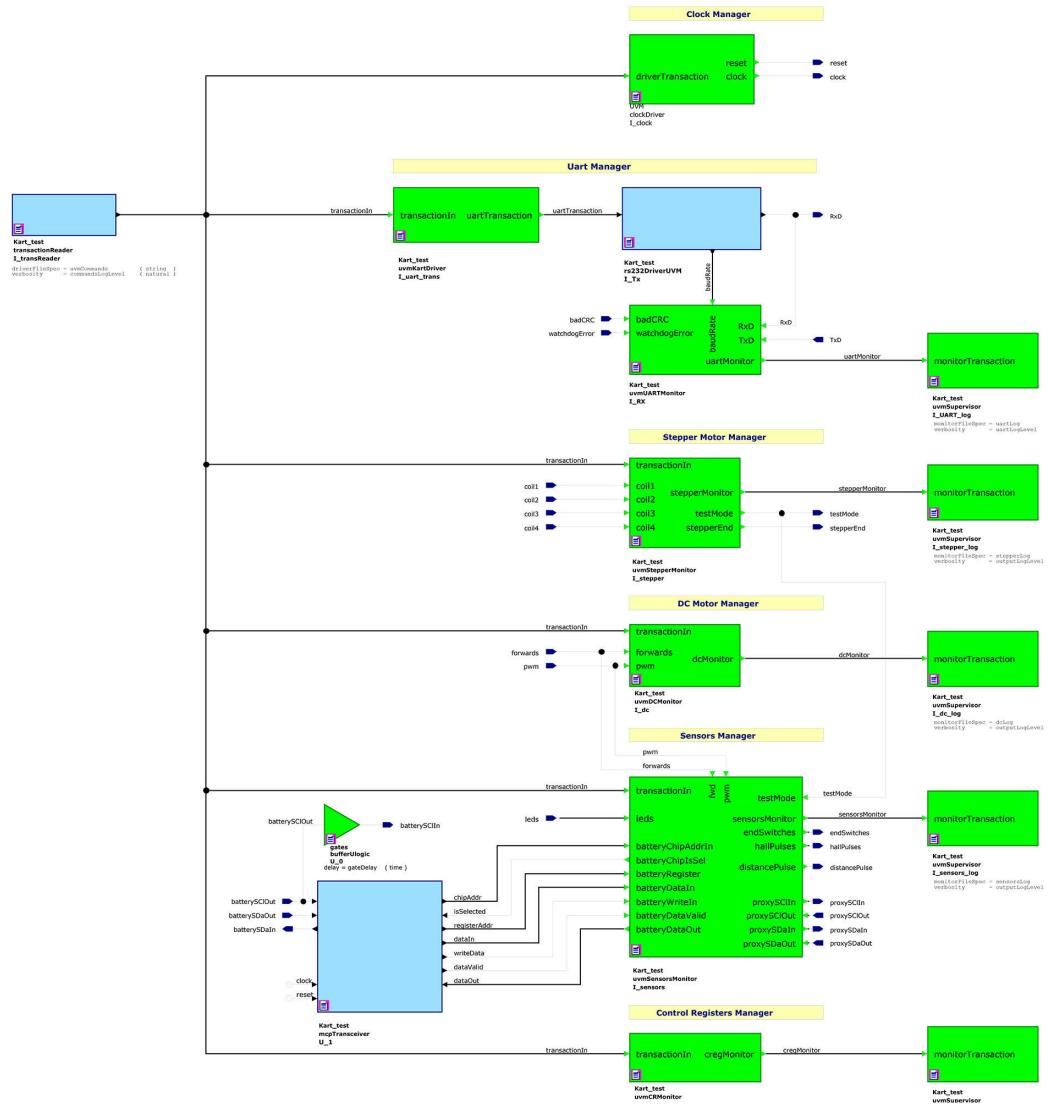


Figure 32: Kart Toplevel Tester

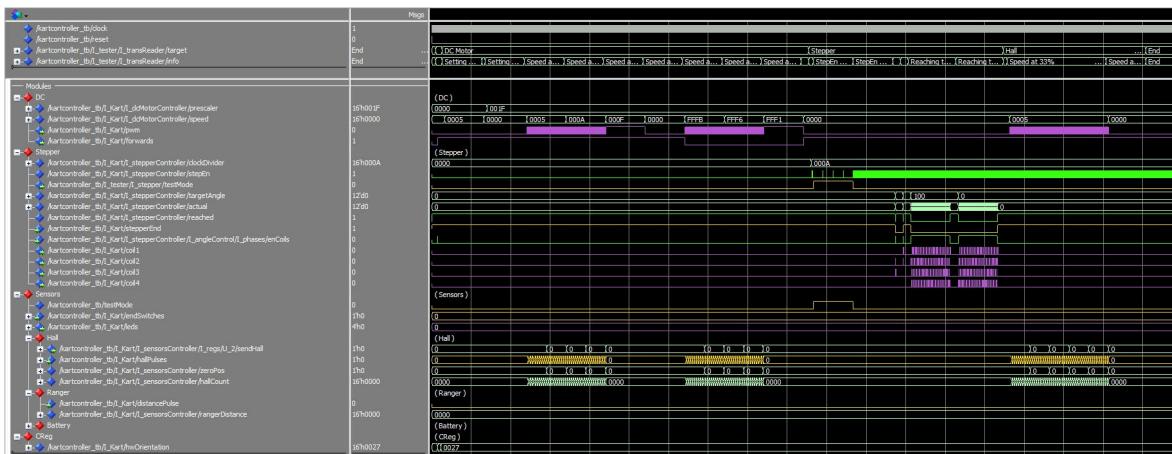


Figure 33: Kart Toplevel Simulation



6.2.1.1 Tests

All the student-designed blocks are tested (check both **target** and **info** signals on the simulation). Contrary to the other testers, there is no direct error logging. One must check the functionality “by hand” in the simulation window (by correlating signals with the info from the transcript window or the log files).

6.2.2 Full-board

Another tester, checking the whole system (including Rx/Tx frames, registers managers ...) can be loaded through the **Kart_test** \Rightarrow **kartController_full_tb** block and the **\$SIMULATION_DIR/Kart/kartStudent.do** file.

It is mostly intended for people developing the full circuit, but left there for curious people:

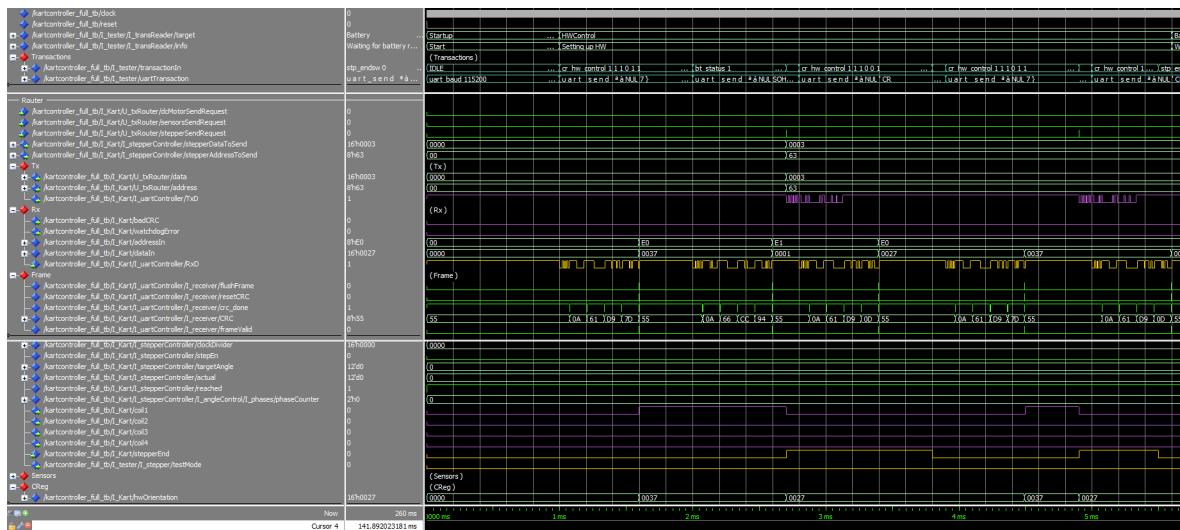


Figure 34: Kart Full Simulation

6.3 Programming the board



Professor validation

Your design must have been validated before any FPGA's programming.

Refer to Appendix A.3 to use and deploy your design thanks to the Libero IDE.



6.4 USB commands emulation



Power Precautions

Use a laboratory power supply limited from 0.05A (no motors) up to 1.2A (with motors).

To test the communication directly from a PC, the tool **EBS3 UART Interpreter** is available in the project folder under **CommandInterpreter** either as a Windows executable, Linux executable or Python script.

Hereafter the steps to follow in order to communicate with the Kart:

- Power the circuit off
- Remove the BLE module - Section 4.7 from the motherboard - Section 4.2
- Power the motherboard - Section 4.2 with a regulated DC voltage supply with +12V
- Wire the USB-C present on the daughterboard - Section 4.3 to your PC
 - Two new UART COM ports should be detected
- Download and/or open the Kart Command Interpreter utility (available in the VHDL project in the folder **CommandInterpreter/**)
 - [Linux](#)
 - [Windows](#)
 - [Source code](#)
- In the top menu **Serial** ⇒ **Port**, select the correct COM port
 - should be the biggest of the two new ports

To test the connection, click the **Read** button. The **Tx** and **Rx** values should change, with **Rx** becoming green (frame correctly received), and a text added to the text area.

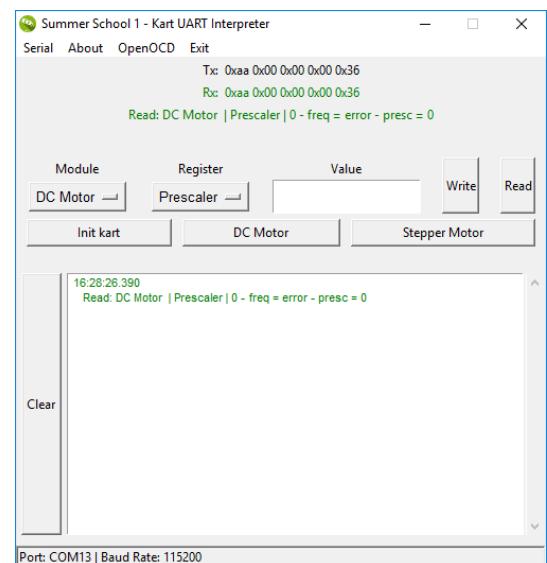


Figure 35: Kart EBS3 UART Interpreter

6.4.1 Quick Test

The simplest way to test both motors are the three following buttons:



Button	Effect	Output
Init Kart	<ul style="list-style-type: none"> Set the DC prescaler, stepper prescaler, and execute the restart sequence. Must be clicked first. Answer the 4 prompts following your hardware configuration. 	Init Kart DC Prescaler to 31 Stepper Prescaler to 500 BT as connected CReg to reset w. stepper end (0b11111) CReg to normal mode (0b100111) Init done
DC Motor	<ul style="list-style-type: none"> Set the speed to full for 2s Set it to 0 for 2s Set it to full in reverse for 2s 	DC test DC speed tp 15 DC speed tp 0 DC speed t0 -15 DC speed to 0 DC test done <i>For karts with mounted hall sensors, extra messages will tell the speed.</i>
Stepper Motor	<ul style="list-style-type: none"> Set the stepper to 400 (30°) Detect angle reached Set the stepper to 0 Detect angle reached 	Stepper test Stepper tp 400 (30°) 10:46:33.169 Read: Stepper Motor Actual Angle 28 ... 10:46:34.804 Read: Stepper Motor Actual Angle 364 10:46:34.999 Read: Stepper Motor Stepper HW stepper open - position reached Stepper to 0 10:46:36.207 Read: Stepper Motor Actual Angle 364 ... 10:46:38.029 Read: Stepper Motor stepper open - position reached Stepper test done

Figure 36: Quick Test buttons

6.4.2 Registers R/W

Each register can be read and/or written by hand following their data description - Section 7.2. For this, select the **Module** first, then which **Register** to access.

Read

To read, simply click the **Read** button. Successful read will be shown in green (CRC is ok) and logged, with extra computed informations. For example the DC prescaler logs the motor frequency.

Write

To write, enter a value in the value box such as:

- Direct integer (*only DC speed should be negative*)
- 0bxxxx** binary values
- 0xxxxx** hexadecimal values

Then click on the **Write** button.



Reset: Simply power-cycle the FPGA board to reset all registers.



7 | Communication

This section defines the serial link protocol [21] used to communicate between the Kart and the BLE Module - Section 4.7 [10] to the PC or Android Smartphone.

Contents

7 Communication	43
7.1 General Principle	44
7.1.1 Serial Port Configuration	44
7.1.2 Message format	44
7.1.2.1 Frame example	44
7.2 Registers	45
7.3 Initialisation Sequence	47
A Tools	48
A.1 HDL Designer	48
A.2 Modelsim	49
A.3 Microchip Libero	50
A.3.1 Overview	50
A.3.1.1 Synthesis	50
A.3.1.2 Flash	50
A.3.2 Synthesis	51
A.3.2.1 Prepare project	51
A.3.2.2 Synthesize	52
A.3.2.3 Bitfile	53
A.3.2.4 Tips	53
A.3.3 Flashing	54
A.3.3.1 FlashPro	54
A.3.3.2 OpenOCD	55
B PMod boards	56
B.1 Inputs	56
B.1.1 Ultrasound Ranger	56
B.1.2 Buttons / Digital Inputs	57
B.2 Outputs	57
B.2.1 PMOD-OD2 board	58
B.2.2 Simple 4 Leds or Digital Outputs	59
B.3 Breadboard	60
C Inspiration	61
Bibliography	66



7.1 General Principle

The system incorporates a BLE module see Section 4.7. To prevent line congestion, data transmission from the Kart to the User occurs exclusively during specific events or upon the User's request. This strategy helps optimize communication by minimizing unnecessary data transfer and enhancing overall system efficiency.

7.1.1 Serial Port Configuration

The module communicates with the FPGA through UART with the following settings:

Reading State	Data bits	Parity	Stop bits	Handshake	Baudrate
HIGH	8	NONE	1	NONE	115'200

Table 1: Serial Port Configuration

7.1.2 Message format

SoF (1byte)	Address (1byte)	Data (2bytes)	EoF (1byte)
0xAA	UINT8	UINT16 / INT16 / VECTOR16 (MSB First)	CRC8 / ITU

Table 2: Message Format

The address is decomposed as follows: 0bMMWRRRRR

- MM : targeted module
 - 0b00 : DC Motor
 - 0b01 : Stepper Motor
 - 0b10 : Sensors
 - 0b11 : Control Registers
- W : defines if the data is saved to ('1') or read from ('0') the FPGA
 - The FPGA will respond to a request with the exact same address when W = '0'
 - The FPGA will save incoming data in the targeted register when W = '1'
 - The FPGA will send data on predefined events with the W bit set to '0'
- RRRRR : targeted register

7.1.2.1 Frame example

For the BLE module to light LED1 with it changing each 500 ms, the following frame is sent:

SoF (1byte)	Address (1byte)	Data High (1byte)	Data Low (1byte)	EoF (1byte)
0xAA	0b10100001	0b10000001	0b11110100	0x74

Table 3: Frame example LED+ 500ms



7.2 Registers

Device	Access	from	to
DC Motor	Read	0x00	0x1F
	Write	0x20	0x3F
Stepper Motor	Read	0x40	0x5F
	Write	0x60	0x7F
Sensors	Read	0x80	0x9F
	Write	0xA0	0xBF
Control	Read	0xC0	0xDF
	Write	0xE0	0xFF

Table 4: Memory Map

Addr	Name	Type	Description	Direction	Event
DC Motor					
0	Prescaler	UINT16	DC PWM frequency f_{PWM} $\frac{f_{\text{clk}}}{\text{PWM_steps} * \text{prescaler}} = \frac{10\text{MHz}}{16 * \text{prescaler}}$		
1	Speed	INT5	Desired speed from -15 (0xFFFF1) to 15 (0x000f) negative = backwards		
Stepper Motor					
0	Prescaler	UINT16	Stepper switching frequency $f_{\text{step}} = 100 \frac{\text{kHz}}{\text{prescaler}}$		
1	Target angle	UINT16	Desired steering angle in motor steps 0 = end switch		
2	Actual angle	UINT16	Actual steering angle in motor steps 0 = end switch		When a delta of at least STP_ANGLE_DELTA_DEG (2°) from the last registered value happens
3	Stepper HW	UINT14	Bit[0] : stepper end + Bit[1]: position reached		Sent when stepper end is pressed (rising edge) or position reached (rising edge)
		Vector2	Bits[15:2]: actual steering angle		

Table 5: Communication Registers (1)



Addr	Name	Type	Description	Direction	Event
Sensors					
0	LED1	BIT + UINT15	Bit[15]: on - off Bits[14:0]: half-period in ms if 0, led status = bit 15		
	LEDx	
7	LED8	BIT + UINT15	Bit[15]: on - off Bits[14:0]: half-period in ms if 0, led status = bit 15		
8	Voltage	UINT16	Battery Voltage $U = \text{register} * 250e^{-6} * 7.8V$		When a delta of at least SENS_BATT_DELTA_MV (50) from the last registered value happens
9	Current	UINT16	Consumed current $I = \text{register} * \frac{250e^{-6}}{100*5e^{-3}}$		When a delta of at least SENS_CURR_DELTA_MA (50) from the last registered value happens
A	Range finder	UINT16	Distance to sensor $D = \text{register} * \frac{25.4}{147e^{-6} * (\frac{10M}{10})}$ Register zeroed if less than 152mm (sensor min distance) or greater than 1500mm (arbitrary max distance) Event not sent in such case		When a delta of at least SENS_RANGEFNDR_MM (60) from the last registered value happens
B	End Switches	Vec-tor16	Sensors current values Right justified (sensor 1 is bit 0)		On any edge change of any sensor
C	Hall 1	UINT16	Hall pulses count Zeroed on overflow of the register		Each SENS_HALL_OLD_SEND_TIMEOUT_MS (100ms) if value changed from last time
D	Hall 2	UINT16	Hall pulses count Zeroed on overflow of the register		Each SENS_HALL_OLD_SEND_TIMEOUT_MS (100ms) if value changed from last time
Control					
0	Hardware Control	Vector6	Bit[0]: when '0', the Kart goes backwards when the motor turns forward Bit[1]: when '1', the Kart turns to the right as the stepper coils go from 1 to 4 Bit[2]: when '1', the angles are measured clockwise Bit[3]: emulates the end switch contact for the stepper motor Bit[4]: restart the stepperMotor module and stop the DC motor when '1'		The end sensor always defines angle 0. Angles are always positive numbers in registers. If bits 1 and 2 are different, the stepper motor phases sequence has to be inverted.
1	BT Status	Vector1	Bit[0]: when '0', the smartphone is disconnected	NRF	The register is set by the NRF itself, since it is not possible to foresee the disconnection. If the bluetooth connection is lost, the kart must stop.

Table 6: Communication Registers (2)



7.3 Initialisation Sequence

Multiple registers must be set before the Kart can drive. The following sequence is used by the EBS3 serial interpreter - Section 6.4 :

- Write **DC Motor** \Rightarrow **Prescaler** to **31** (around 21 kHz PWM frequency)
- Write **Stepper Motor** \Rightarrow **Prescaler** to **400** (250 Hz coil switching frequency)
- Tell the smartphone it is connected by writing **Control Registers** \Rightarrow **BT status** to **1**
- Write **Control Registers** \Rightarrow **Hardware Control** to **0b10xxx** to restart the system
 - ▶ The stepper should turn until hitting the end switch, except if already on it
- Read **Stepper Motor** \Rightarrow **Stepper HW** and check the last bit
 - ▶ If is '1', it means we are already zeroed
 - ▶ If not, wait for an event from this register to tell the reset is complete
- Write **Control Registers** \Rightarrow **Hardware Control** to **0b00xxx** to deassert the reset

The Kart is now ready to function !



The **Control Registers** \Rightarrow **restart bit** is automatically reset back to '0' when the **stepper_end** input is activated.



A | Tools

A.1 HDL Designer

Mentor HDL designer is the tool for graphical design entry as used during laboratories [4]


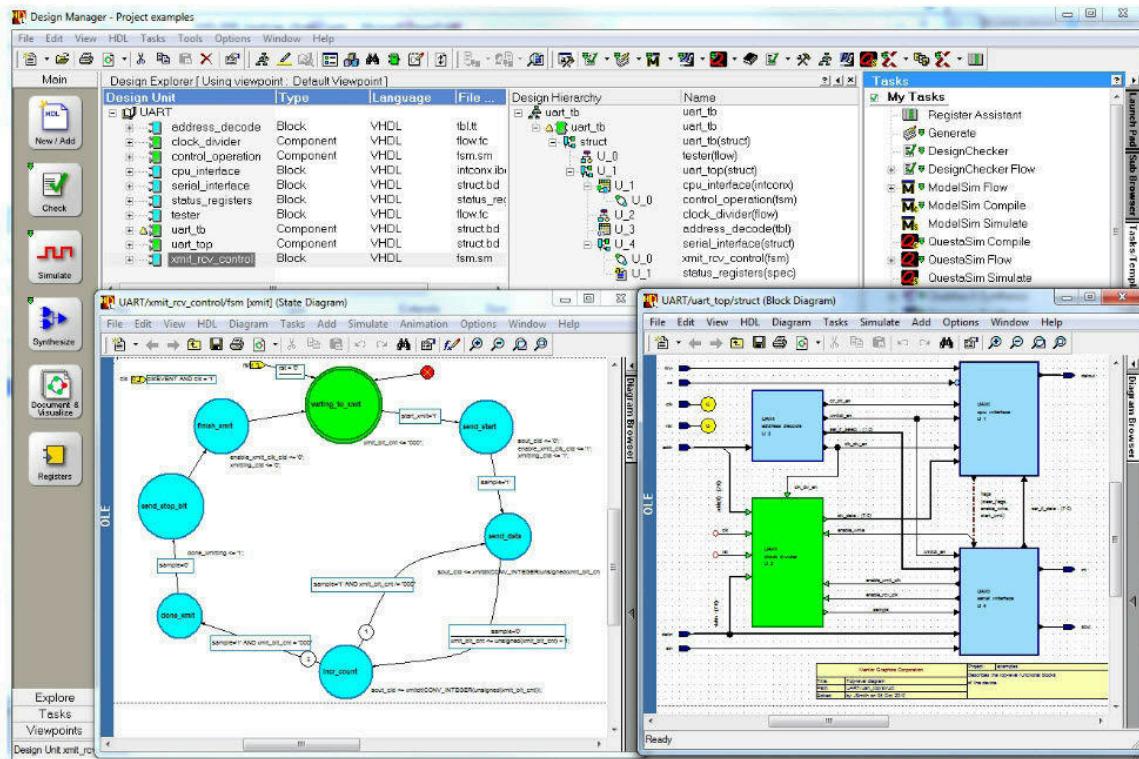


Figure 37: Mentor HDL Designer

Always run the **kart.bat** file to launch the project.

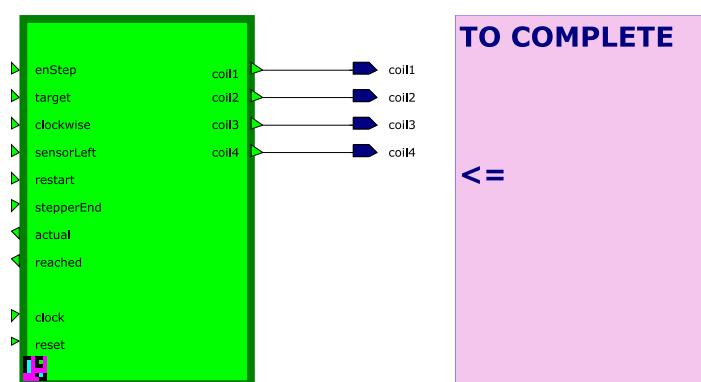Parts you must complete are pointed by **purple text blocks**:



A cheatsheet is available online under https://github.com/hei-synd-ss1/ss1-docs/blob/main/control-electronics/EDA_Tools_Cheatsheet.pdf.



A.2 Modelsim

Mentor ModelSim for simulation [5]

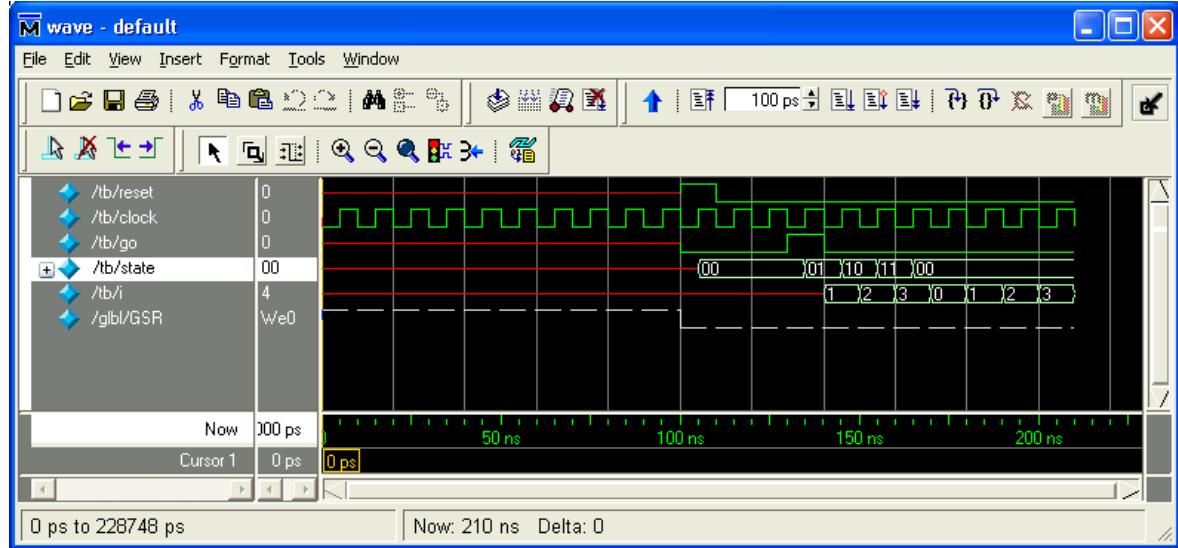


Figure 38: Mentor Modelsim

The simulations are explained under Section 6. They allow to test on the module level itself or the complete circuit in operation by simulating commands received from the smartphone.

The simulations files are available under the **Simulation** folder and contains among others the **.do** waveforms files related to all VHDL tester.



A.3 Microchip Libero

Microchip Libero IDE for synthesis and programming[6]

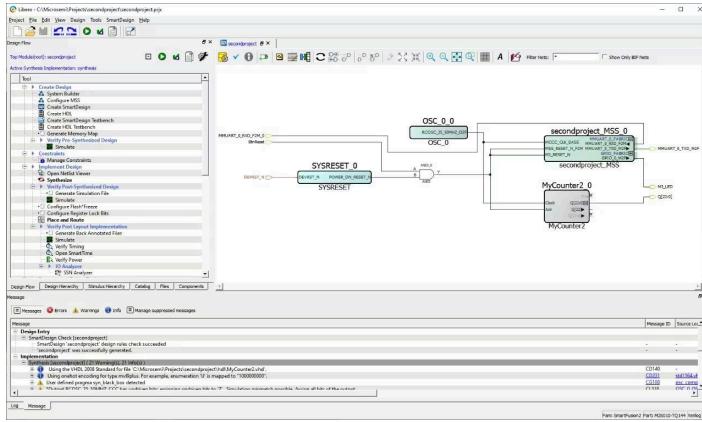


Figure 39: Microchip Libero

Libero SoC is a design software from Microchip (former Actel) for FPGA.

A.3.1 Overview

A.3.1.1 Synthesis

Libero SoC can be launched as a standalone or from one of its *.prjx project file to complete the synthesis process.

One can launch Libero directly from the Kart project by running the correct task.

- On HDL Designer, open the **Board** library
- Highlight the top-level block **Kart_Board**
- On the tasks list on the right, first run **Prepare for synthesis** then **Libero Project Navigator**

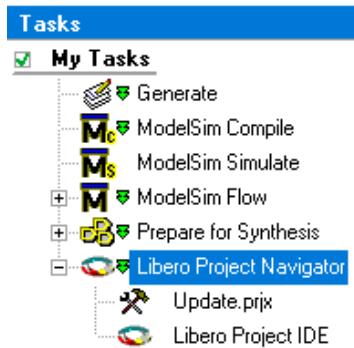


Figure 40: HDL Designer - Tasks

A.3.1.2 Flash

The FPGA flash is done through the FlashPro software included with Libero through the generated *.pdb bitfile thanks to a dedicated programmer such as the FlashPro4.

It can be launched as a standalone or directly from within Libero.

FlashPro can also be used to generate *.svf files which can then be used with OpenOCD to flash the FPGA by its USB port.



A.3.2 Synthesis

A.3.2.1 Prepare project

After running the HDL task, the project window opens. On the list located on the left, locate the **Compile** \Rightarrow **Constraints** \Rightarrow **yourConstraintsFile.pdc** \Rightarrow right-click \Rightarrow **Mark as used**:

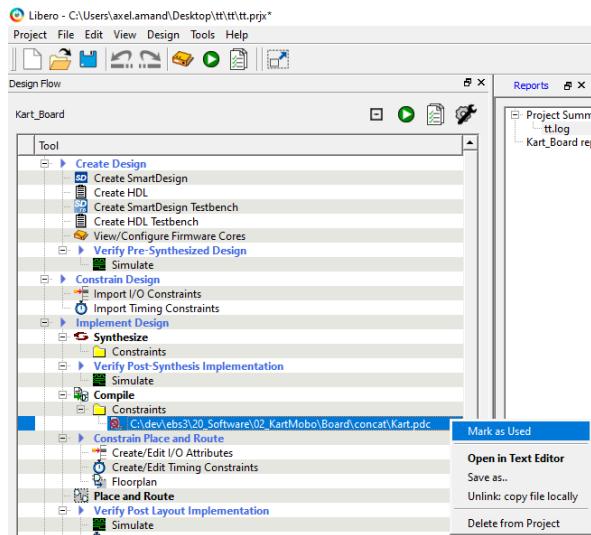


Figure 41: Libero - Use constraints

Right click on **Synthesize** \Rightarrow **Open Interactively**. In the newly opened window, on the left, set the correct clock frequency and exit while saving:

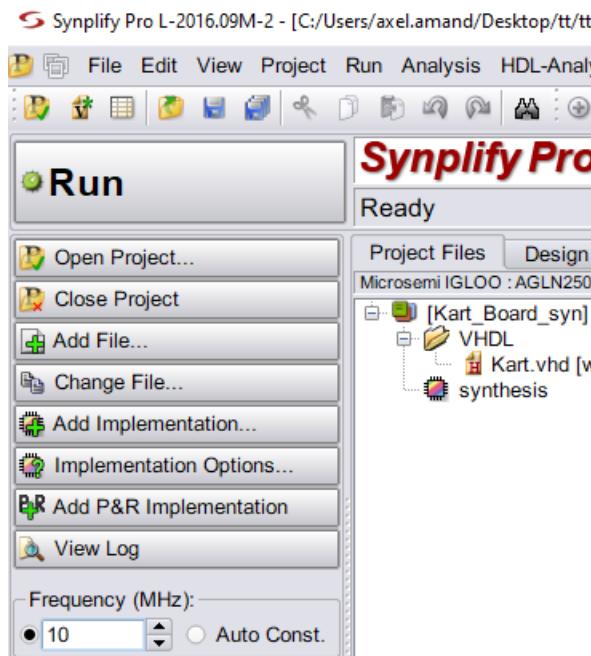


Figure 42: Libero - Clock setup

This step is required for the program to estimate if the implementation reaches the correct timings.

Right click on **Compile** \Rightarrow **Open Interactively** \Rightarrow **I/O attribute editor** and check that pins are correctly linked to the internal signals with correct settings:

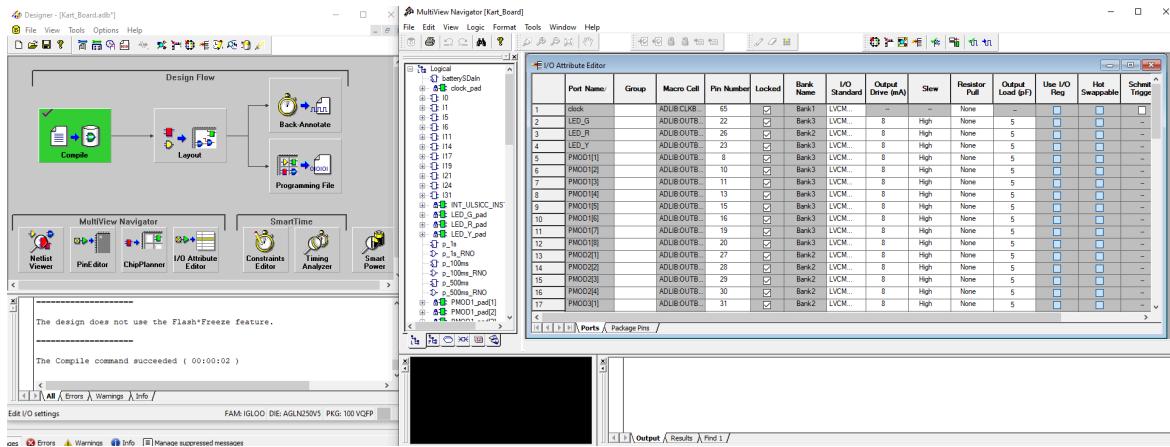


Figure 43: Libero - Constraints check

A.3.2.2 Synthesize

When the project is ready, the VHDL file must be synthesized, compiled and rooted on the chip.

Either click on **Layout** in the previously opened window (**Compile** ⇒ **Open Interactively** ⇒ **Layout** ⇒ **Ok**) or double click on **Place and Route** in the task list.

The **Message** window on the bottom of Libero can be used to check for errors and warning (both should always be checked). Some parts of the circuit may be pruned, clocks inferred unintentionally, unused signals found ...

In addition, reports can be browsed in the **Reports** tab, notably:

- **Synthesize - prjName.srr:**

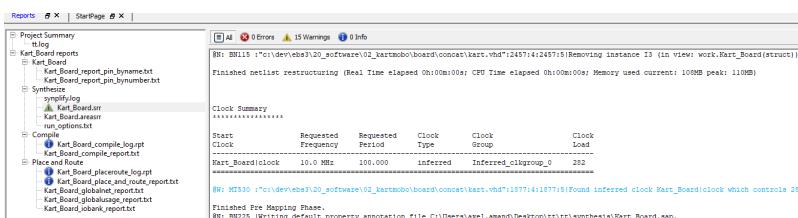


Figure 44: Libero - Logfile

which contains informations on:

- **Clock summary:** should only show the actual clocks - if some inferred ones are found, there is a design problem in the VHDL code
- **Performance summary:** shows the worst slacks, if the timings are met and the potential fastest clock usable
- **Core Cells and RAM/ROM usages:** how full the FPGA is
- **Compile - prjName_compile_log.rpt** shows the following:
 - **Compile Report:** more detailed view of used cells, BRAM block, I/Os ...
 - **I/O Technology:** ensure the standard is set to **LVC MOS33**
 - **I/O Placement:** ensure I/Os are all locked (Placed and UnPlaced ones may indicate errors or that the compilation used a pad to root a signal more easily because said pad was not locked even if not used ⇒ user must ensure the pad is not rooted to anything on the board or lock it beforehand)



- **Place and Route - prjName_globalnet_report.txt** shows global clocks and reset signals found under **Nets Sharing Loads**. In most cases, only a clock and a reset should be shown.

A.3.2.3 Bitfile

If the compilation is successfull, double click on **Generate Programming Data** to generate a *.pdb bitfile.

FlashPro can be launched directly with a right click on **Program Device** ⇒ **Open Interactively**.

A.3.2.4 Tips

Locked pins

All I/Os referenced in the VHDL file should be linked to a pad of the chip. If when trying to compile the following window appears, the *.pdc constraints file may be missing some I/Os:

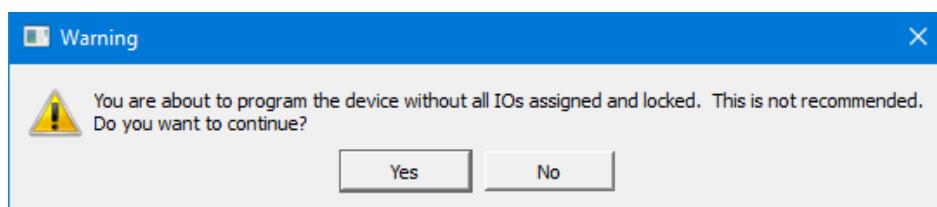


Figure 45: Libero - PDC warning

Click No and correct it.

Inferred clocks

Incorrect designs may lead the synthesizer to infer some clocks (e.g. may appear on state machines depending on a signal to trigger each state).

If the warning is ignored, it may replace the clock with said signal. Incorrect behavior may result (desynchronized state changed, no state changes at all ...). Here is an example of inferred clock:

Clock Summary					
Start Clock	Requested Frequency	Requested Period	Clock Type	Clock Group	Clock Load
Kart_Board clock	10.0 MHz	100.000	inferred	Inferred_clkgroup_0	1328
coilControl stepdelayed_inferred_clock	10.0 MHz	100.000	inferred	Inferred_clkgroup_1	4

Figure 46: Libero - PDC warning



A.3.3 Flashing

A.3.3.1 FlashPro

Overview

FlashPro is the official tool supported for the Karts FPGA. *It is required to create compatible programming files for OpenOCD*

Usage Launch FlashPro directly or from within the Libero project with a right click on **Program Device** \Rightarrow **Open Interactively**.

Wire a compatible programmer (such as a FlashPro4) and click on **Refresh/Rescan for Programmers** which should show found devices:

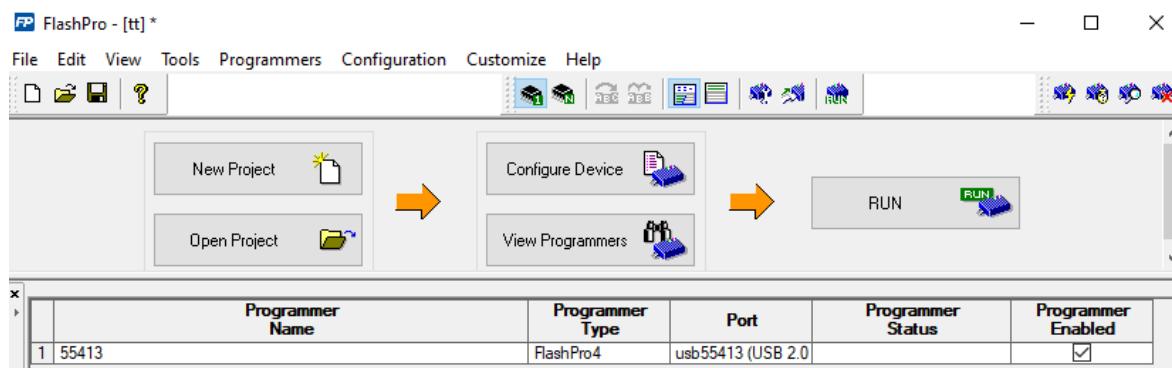


Figure 47: Flashpro - Programmers

Under **Configuration** \Rightarrow **Load Programming File** select the previously created *.pdb file.

Wire the board, connect the programmer, then click on **PROGRAM**. The advancement is shown in column **Programmer Status**.



The programmer does not supply the daughterboard with power. An external power source (motherboard or USB-C) is needed.



I/Os states normally remain in high-impedance state (with potential pull resistors) while the chip is being programmed. For sensitive applications, disconnect it from the motherboard beforehand.



A.3.3.2 OpenOCD

The board can be programmed without any third-parties hardware through [OpenOCD](#) thanks to the embedded FT2232HL chip on the daughterboard which offers both an UART and a JTAG interface.



This method is not currently supported by your teachers. You have no guarantee to receive any help from them.

If interested, refer to the [doc/Kart_AGLN250.pdf](#) - section **OpenOCD**.

To not run flash commands by hand, once OpenOCD is installed correctly with its extension files and added to the path, you can run the **EBS3 UART Interpreter** - Section 6.4 and click on **OpenOCD** in the toolbar. Select any of your **.svf** file for the tool to locate all required files. It will then launch the programming and logs are output in the textbox.



B | PMod boards

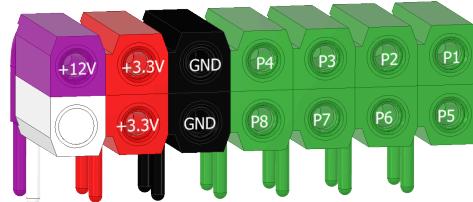


Figure 48: PMOD Pinning [22], [9]

B.1 Inputs



The sink per pin cannot be higher than 8 mA.
Never ever input a voltage different than +3.3V. Internal pull-up/down can be enabled at will on the FPGA.

B.1.1 Ultrasound Ranger

An ultrasound ranger can detect if there is an obstacle at the front or back of the kart. It is based on the PMOD-MAXSONAR board from Digilent [23], and can be plugged into any one-row PMOD connector.



Figure 49: PMOD MAXSONAR



No internal pull resistor should be enabled on the FPGA side.
Beware not to wire it on the +12V pin !

See Section 5.3.3 for more informations on the generated pulse.



B.1.2 Buttons / Digital Inputs

The **PMOD-CON1** - *Wire terminal connectors* - and the **PMOD-TPH** - *Pin headers* - can both be used to interface digital inputs.

[24], [25]

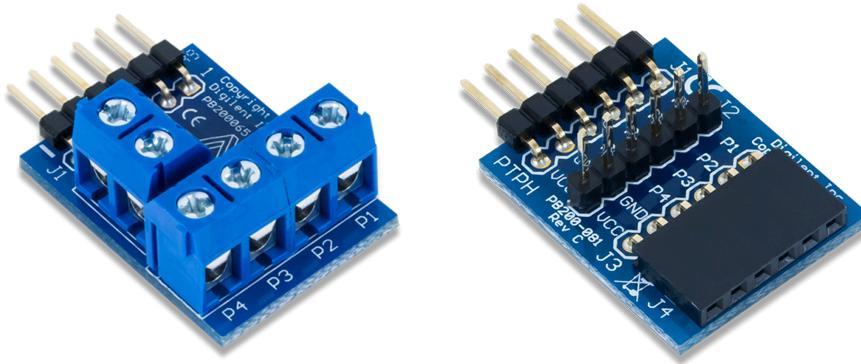


Table 7: PMOD-CON1 and PMOD-TPH boards

The first connects inputs thanks to screw terminals, the second with pin headers.



Enable pull resistors on the FPGA side based on your input type (push-pull, open-drain ...).

B.2 Outputs




The source or sink per pin cannot be higher than 8 mA.
The outputs are always in the +3.3V range and there is no voltage feedback protection !



B.2.1 PMOD-OD2 board

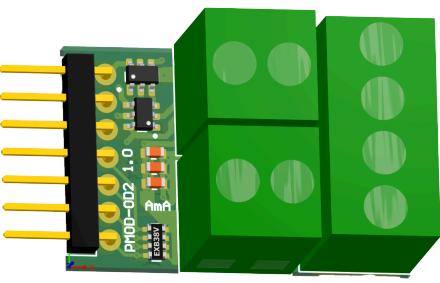The **PMOD-OD2** is a custom board allowing to control up to 4 outputs with a selectable voltage level thanks to open-drain outputs.



Pin	Descr.
7	P1 NC
6	P2 NC
5	P3 NC
4	P4 NC
3	GND
2	3.3V
1	12V

Table 8: PMOD DC-Stepper Control board and pinning

The voltage is selected by soldering one of the three following resistors on the backside of the board to switch between **+3.3V**, **+5V** or **+12V**:



Table 9: Vio selection

There are three screw terminals:

- A double terminal for Vio
- A double terminal for GND
- A quad terminal for the four outputs

They are all indicated on the back of the board.

Wiring loads

Since outputs are open-drains, two wiring methods can be used:

- **Loads driving:** to simply drive loads like LEDs, sensors power ... they must simply be wired between the Vio screw terminal and the load screw terminal
- **Pseudo push-pull:** hardware which require digital inputs (like a servo control pin) need either à ‘1’ or a ‘0’. As is, the circuit can only output a ‘0’ or a ‘Z’. To counter that, either add a resistor between the Vio screw terminal and the load screw terminal, or solder one of the **R2 to R5** resistor on the back of the board

Both methods are shown in Figure 50 :



Output

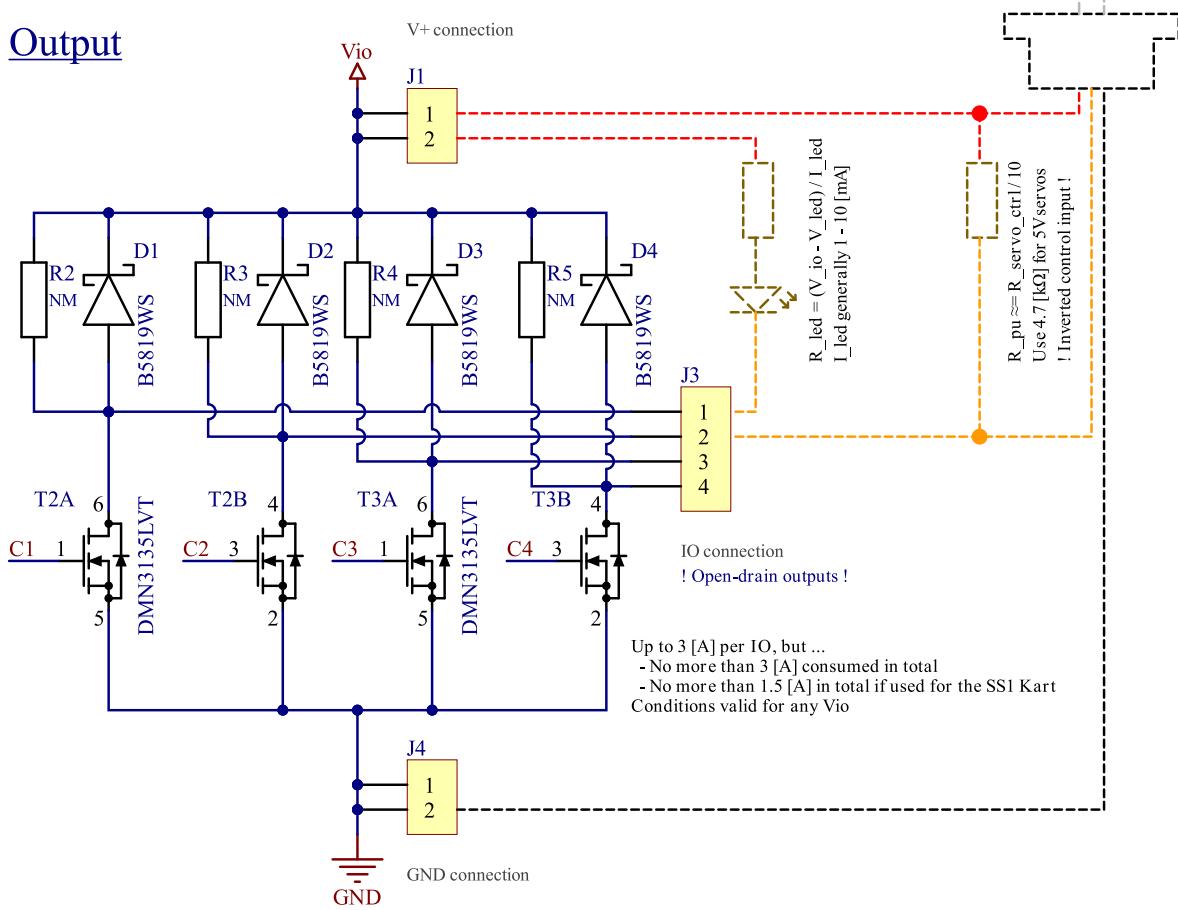


Figure 50: Driving loads with PMOD-OD2

B.2.2 Simple 4 Leds or Digital Outputs

The **PMOD-OD1** - *Open-drain outputs* - allow to interface digital outputs to the Kart with up to 3A per pin.



It is not possible to drive more than arnd. 1.5A in TOTAL because of the daughter-board's alimentation characteristics.



Table 10: PMOD-OD1 boards

B.3 Breadboard

The **PMOD-BB** board is intended for tests. It is a small breadboard which allows to plug components in and test a small circuit before designing a custom circuit.

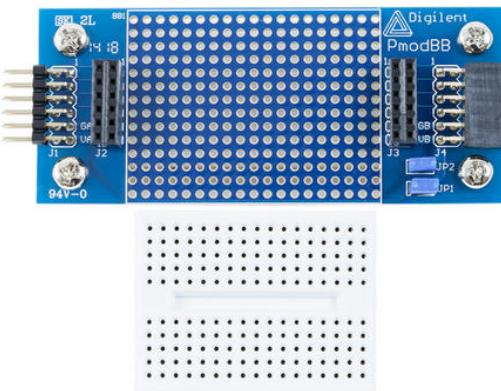


Figure 51: PMOD Breadboard



Use the given breadboard and do not solder on the holes directly.



C | Inspiration

Hes-SO VALAIS
Haute Ecole d'Ingénierie π
Hochschule für Ingenieurwissenschaften

Kart
SummerSchool '04



Figure 52: Summerschool 2004

Hes-SO VALAIS
Haute Ecole d'Ingénierie π
Hochschule für Ingenieurwissenschaften

Kart
SummerSchool '05

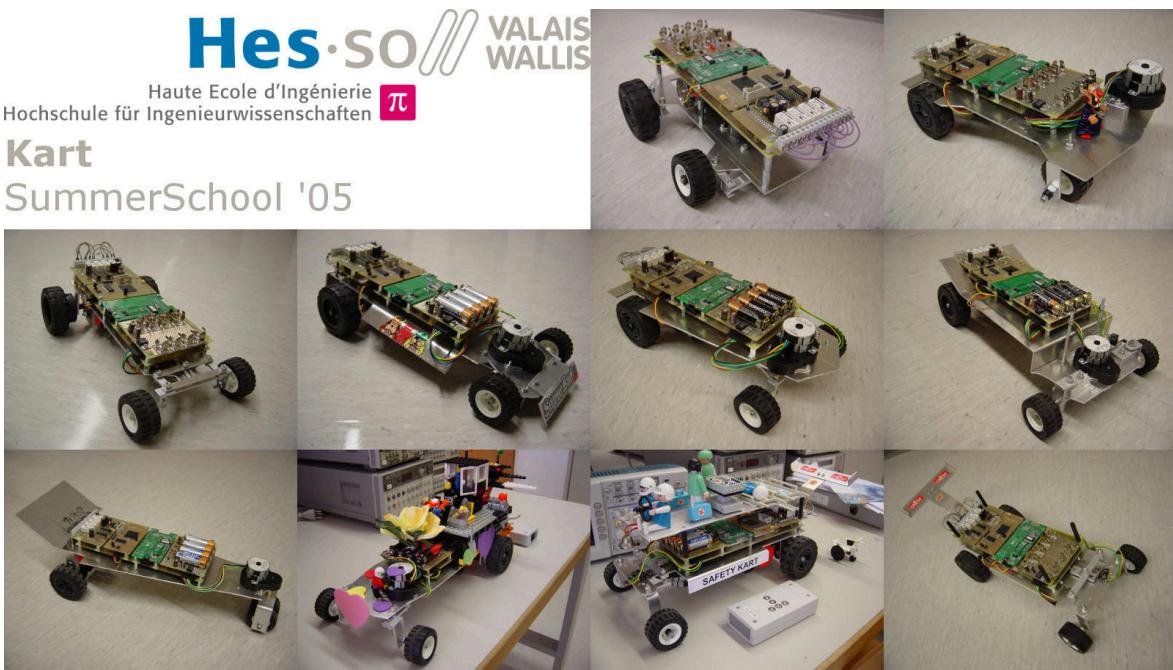


Figure 53: Summerschool 2005



Figure 54: Summerschool 2009

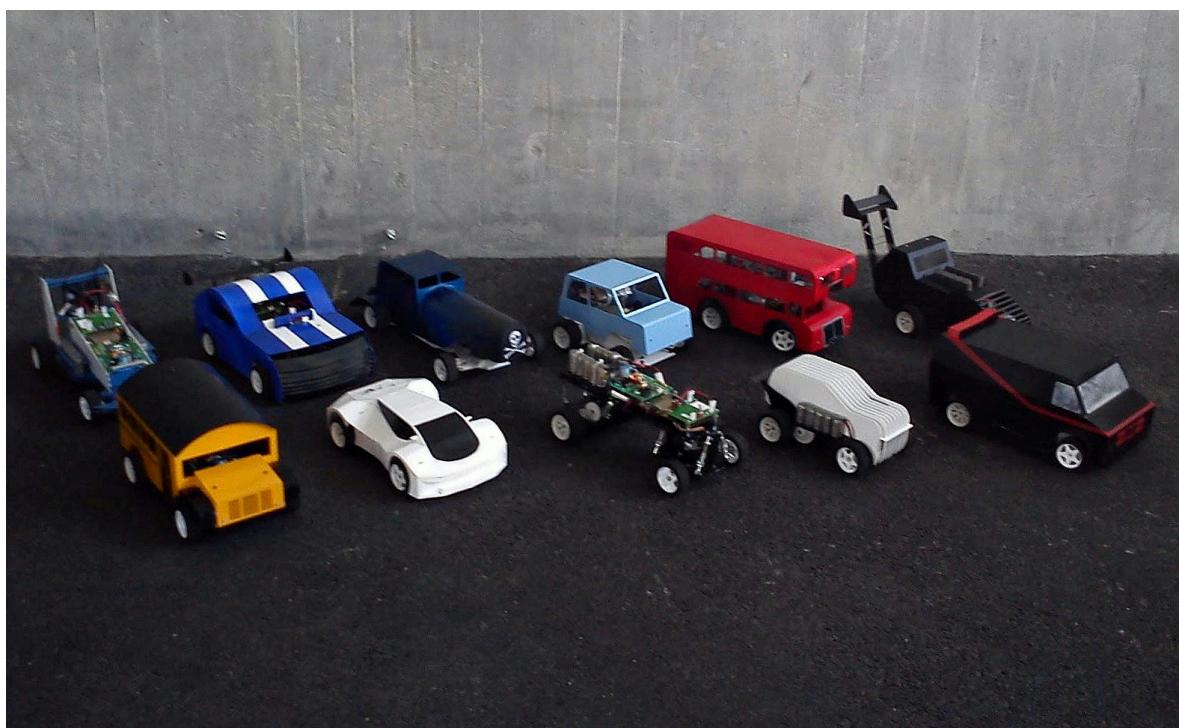


Figure 55: Summerschool 2012



Figure 56: Summerschool 2013



Figure 57: Summerschool 2015

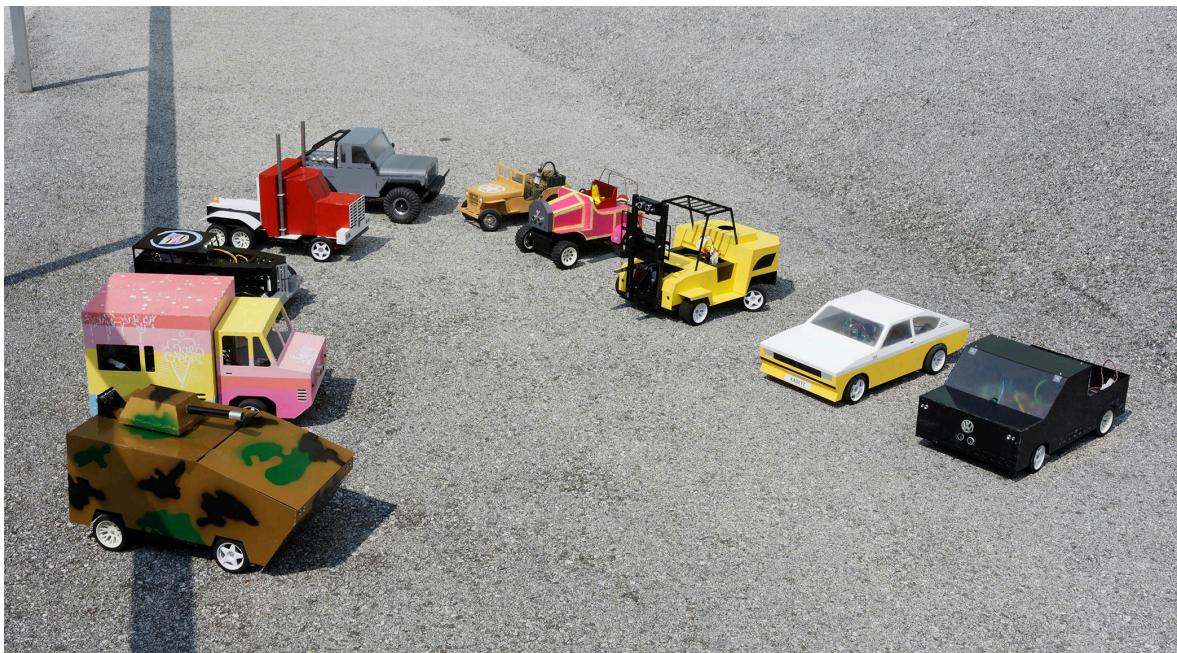


Figure 58: Summerschool 2017



Figure 59: Summerschool 2018



Figure 60: Summerschool 2020



Figure 61: Summerschool 2022



Figure 62: Summerschool 2023



Bibliography

- [1] S. ye industrial, "DC Motor Modelcraft RB350018-2A723R 12V Technical Datasheet." 2006.
- [2] A. Amand and S. Zahno, "FPGA-EBS3 Electornic Technical Documentation." 2022.
- [3] "Hei-Synd-SS1/ss1-vhdl: HEVS SS1 Kart Summerschool Project Based on the EBS3 Igloo Board.." Accessed: Sep. 01, 2023. [Online]. Available: <https://github.com/hei-synd-ss1/ss1-vhdl>
- [4] "HDL Designer Visualizing Complex RTL Designs." Accessed: Sep. 01, 2023. [Online]. Available: <https://eda.sw.siemens.com/en-US/ic/hdl-designer/>
- [5] "ModelSim HDL Simulator." Accessed: Sep. 01, 2023. [Online]. Available: <https://eda.sw.siemens.com/en-US/ic/modelsim/>
- [6] "Libero® IDE | Microchip Technology." Accessed: Sep. 01, 2023. [Online]. Available: <https://www.microchip.com/en-us/products/fpgas-and-plds/fpga-and-soc-design-tools/fpga/libero-ide>
- [7] "IGLOO Nano Low Power Flash FPGAs with Flash*Freeze Technology Datasheet." 2019.
- [8] M. Technologies, "Microchip MCP3426/7/8, 16-Bit, Multi-Channel $\Delta\Sigma$ Analog-to-Digital Converter with I²C/TM Interface and On-Board Reference." 2009.
- [9] D. Inc, "Digilent Pmod Inteface Specification v1.2.0." 2017.
- [10] "nRF52840 Dongle." Accessed: Sep. 01, 2023. [Online]. Available: <https://www.nordicsemi.com/Products/Development-hardware/nRF52840-Dongle>
- [11] F. INC, "FTDI FT2232H Dual High Speed USB to Multiporpouse UART/FIFO IC." 2019.
- [12] A. Amand and S. Zahno, "Kart SODIMM-200 Pinning." 2022.
- [13] "Pulse-Width Modulation." Aug. 29, 2023. Accessed: Sep. 15, 2023. [Online]. Available: https://en.wikipedia.org/w/index.php?title=Pulse-width_modulation&oldid=1172794179
- [14] "H-Bridge." Aug. 07, 2023. Accessed: Sep. 15, 2023. [Online]. Available: <https://en.wikipedia.org/w/index.php?title=H-bridge&oldid=1169162530>
- [15] N. Inc, "Nanotec SP3575M0906-A Stepper Motor Datasheet." 2006.
- [16] D. Inc, "Digilent Pmod DC Stepper Schematic." 2022.
- [17] Omron, "Datasheet Omron Subminiature Basic Switch Offers High Reliability and Security." 2005.
- [18] Honeywell, "Honeywell SS311PT/SS411P Bipolar Hall-effect Digital Position Sensors with Build-in Pull-up Resistor." 2009.
- [19] "Schmitt Trigger." Aug. 28, 2023. Accessed: Sep. 15, 2023. [Online]. Available: https://en.wikipedia.org/w/index.php?title=Schmitt_trigger&oldid=1172685652
- [20] N. Semiconductor, "Datasheet Nordic NRF52840 Dongle." 2020.
- [21] "Universal Asynchronous Receiver-Transmitter." Aug. 28, 2023. Accessed: Sep. 01, 2023. [Online]. Available: https://en.wikipedia.org/w/index.php?title=Universal_asynchronous_receiver-transmitter&oldid=1172648211



- [22] “Pmod™ - Digilent Reference.” Accessed: Sep. 01, 2023. [Online]. Available: <https://digilent.com/reference/pmod/start>
- [23] D. Inc, “Pmod MAXSONAR Reference Manual.” 2014.
- [24] D. Inc, “Digilent Pmod CON3 Schematic.” 2015.
- [25] D. Inc, “Pmod CON3 Reference Manual.” 2016.